




intro to electrical quiz 2

ical quiz 2

IMG-20140326-WA0008 - Windows Photo Viewer

https://www.dropbox.com/lightbox/home/MAU009 Intro to Electrical Circuits %26 Electronic Devices/Quiz 2

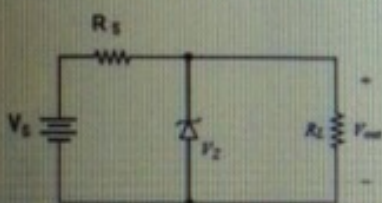Find the minimum value of R_L for which the output voltage keeps exactly at V_Z .



Given $V_S = 25\text{ V}$, $V_Z = 15\text{ V}$, and $R_S = 25\text{ K}\Omega$.

- ☐ 35.0 $\text{K}\Omega$
- ☐ 20.5 $\text{K}\Omega$
- ☒ 37.5 $\text{K}\Omega$
- ☐ 25.0 $\text{K}\Omega$

Moving to the next question prevents changes to this answer.


Question 2 of 5

IMG-20140326-WA0009 - Windows Photo Viewer

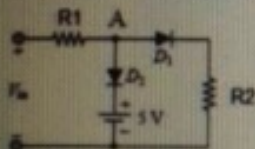Question 1

20 points ☒ Saved

Two ideal diodes are connected in a circuit shown in the figure. Calculate the voltage range of V_{in} so that D_1 is "ON" but D_2 is "OFF".



Given $R1 = 9 \text{ k}\Omega$ and $R2 = 12 \text{ k}\Omega$.


- ☐ $0 < V_{in} < 7.75 \text{ V}$
☒ $0 < V_{in} < 8.75 \text{ V}$
☐ $0 < V_{in} < 7.25 \text{ V}$
☐ $0 < V_{in} < 8.25 \text{ V}$

Moving to the next question prevents changes to this answer.

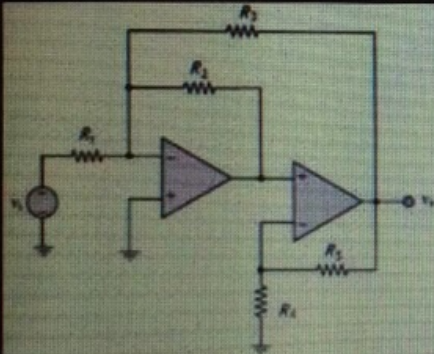Question 1 of 5

IMG-20140326-WA0007 - Windows Photo Viewer

[https://www.dropbox.com/lightbox/home/MA2009 Intro to Electrical Circuits %26 Electronic Devices/Quiz 2](https://www.dropbox.com/lightbox/home/MA2009%20Intro%20to%20Electrical%20Circuits%20%26%20Electronic%20Devices/Quiz%202)



Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=30\Omega$.

- ☐ $A_v = -2.25(V/V)$
- ☐ $A_v = 0.80(V/V)$
- ☒ $A_v = -0.80(V/V)$
- ☐ $A_v = 2.25(V/V)$

IMG-20140326-WA0006 - Windows Photo Viewer




https://www.dropbox.com/lightbox/home/MA2009 Intro to Electrical Circuits %26 Electronic Devices/Quiz 2

Given the circuit of the figure, determine the base current I_{BQ} and collect voltage V_{CEQ} . Assume a 0.6 V offset voltage, $\beta = 50$, and $V_S = 5$ V.

Given $R_1=100 \text{ k}\Omega$, $R_2=200 \text{ k}\Omega$, and $R_3=500\Omega$.

- ☐ $I_{BQ}=0.032\text{mA}$, $V_{CEQ}= 3.350\text{V}$.
- ☒ $I_{BQ}=0.041\text{mA}$, $V_{CEQ}= 3.975\text{V}$.
- ☐ $I_{BQ}=0.041\text{mA}$, $V_{CEQ}= 3.350\text{V}$.

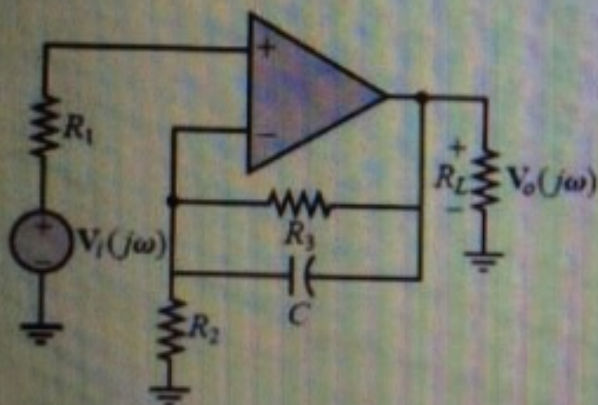The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_V) of the filter.



Given $R_1=2\text{k}\Omega$, $R_2=5\text{k}\Omega$, $R_3=50\text{k}\Omega$, $C=100\text{nF}$.

- ☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_V = 8.22 \text{ dB}$.
- ☒ $\omega_0 = 200 \text{ rad/sec}$; $A_V = 20.83 \text{ dB}$.
- ☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_V = 20.83 \text{ dB}$.
- ☐ $\omega_0 = 200 \text{ rad/sec}$; $A_V = 8.22 \text{ dB}$.

●●●●● StarHub



10:44 pm

🕒 42% 🔋

< Zi Yan

22 of 23

All Media

X

Remaining time: 16 minutes, 59 seconds

Question 3

Given the circuit of the figure, determine the base current I_{BQ} and collector voltage V_{CEQ} . Assume a 0.7 V diode voltage, $\beta = 100$, and $V_{BE} = 0.7\text{ V}$.

Given $R_1 = 10\text{ k}\Omega$, $R_2 = 20\text{ k}\Omega$, and $R_3 = 10\text{ k}\Omega$.


- ☐ $I_{BQ} = 0.01\text{ mA}$, $V_{CEQ} = 4.16\text{ V}$
- ☐ $I_{BQ} = 0.005\text{ mA}$, $V_{CEQ} = 3.72\text{ V}$
- ☐ $I_{BQ} = 0.01\text{ mA}$, $V_{CEQ} = 3.72\text{ V}$
- ☐ $I_{BQ} = 0.005\text{ mA}$, $V_{CEQ} = 4.16\text{ V}$

IMG-20140325-WA0005 - Windows Photo Viewer

Remaining Time: 14 minutes, 34 seconds.

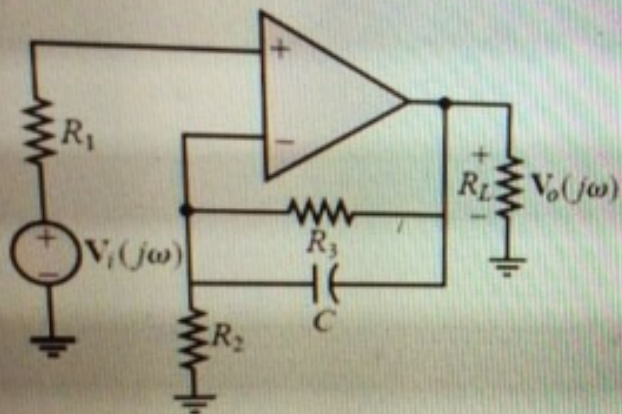Question Completion Status:

The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_V) of the filter.



Given $R_1=2k\Omega$, $R_2=5k\Omega$, $R_3=10k\Omega$, $C=100nF$.


- ☐ $\omega_0 = 2000 \text{ rad/sec}$, $A_V = 9.54 \text{ dB}$
- ☐ $\omega_0 = 2000 \text{ rad/sec}$, $A_V = 7.63 \text{ dB}$
- ☐ $\omega_0 = 1000 \text{ rad/sec}$, $A_V = 9.54 \text{ dB}$
- ☐ $\omega_0 = 1000 \text{ rad/sec}$, $A_V = 7.63 \text{ dB}$





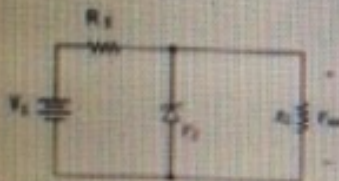Question 2

Find the minimum value of R_1 for which the output voltage keeps exactly at V_2 .



Given $V_1 = 10\text{ V}$, $V_2 = 4\text{ V}$, and $R_L = 25\text{ k}\Omega$

- ☒ 20.0 k Ω
- ☐ 25.0 k Ω
- ☐ 10.0 k Ω
- ☐ 15.0 k Ω

Warning: This question previously changed to this answer.

CANT SEE

IMG-20140325-WA0006 - Windows Photo Viewer

StarHub


10:44 pm

42%

< Zi Yan

20 of 23

All Media

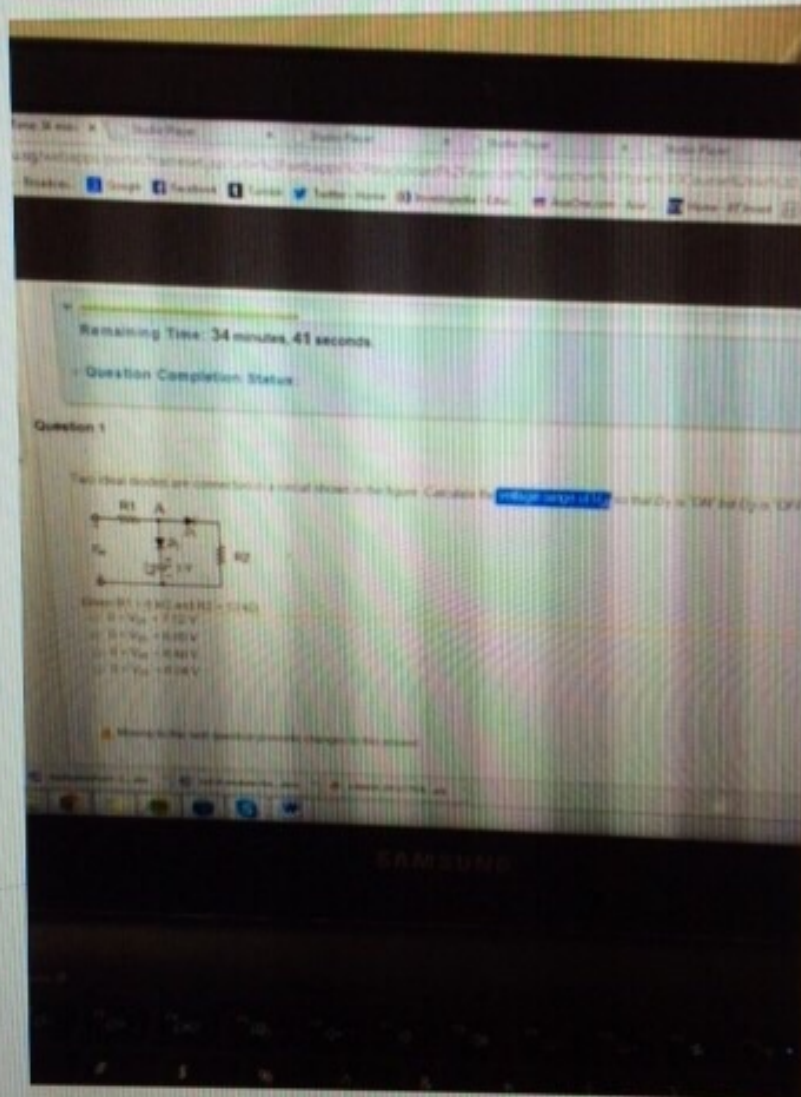

You on 7/11/13 4:26 pm




Remaining Time: 16 minutes, 34 seconds.

Ques

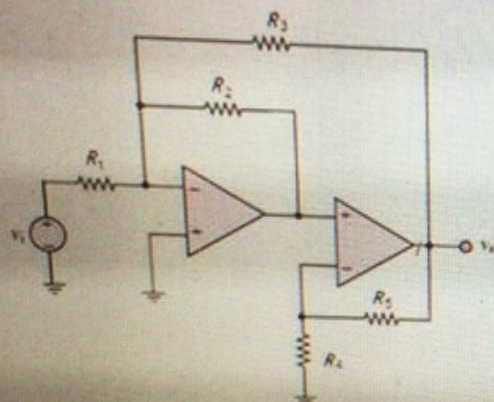Question Completion Status:


If the op-amps in the following circuit are ideal, calculate the overall voltage gain of the circuit $A_V = V_O/V_I$.



Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=20\Omega$ and $R_5=10\Omega$.

- ☐ $A_V = -5.25$ (V/V)
- ☒ $A_V = 0.6$ (V/V)
- ☐ $A_V = -0.6$ (V/V)
- ☐ $A_V = 5.25$ (V/V)

SAMSUNG

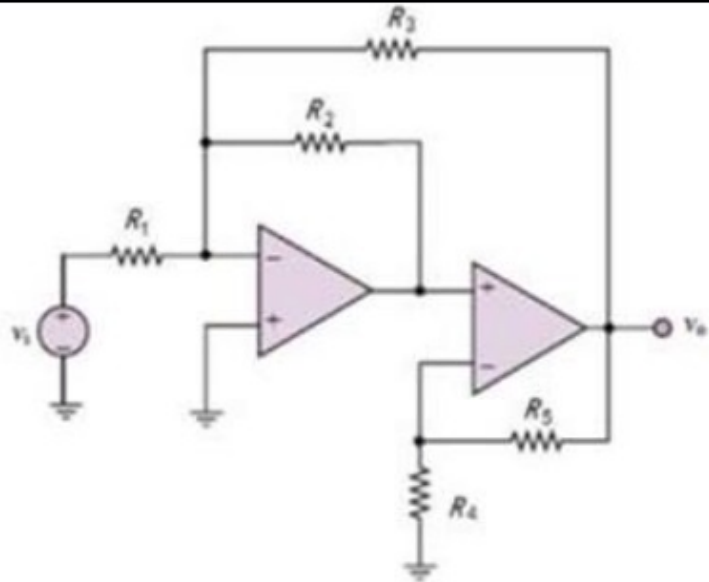


Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=30\Omega$.

- ☐ $A_v = -2.25(V/V)$
- ☐ $A_v = 0.80(V/V)$
- ☒ $A_v = -0.80(V/V)$
- ☐ $A_v = 2.25(V/V)$



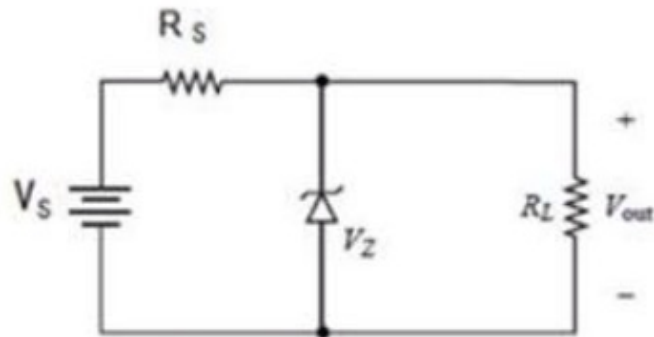Find the minimum value of R_L for which the output voltage keeps exactly at V_Z .




Given $V_S = 25\text{ V}$, $V_Z = 15\text{ V}$, and $R_S = 25\text{ K}\Omega$.

- ☐ 35.0 $\text{K}\Omega$.
- ☐ 20.5 $\text{K}\Omega$.
- ☒ 37.5 $\text{K}\Omega$.
- ☐ 25.0 $\text{K}\Omega$.

 Moving to the next question prevents changes to this answer.

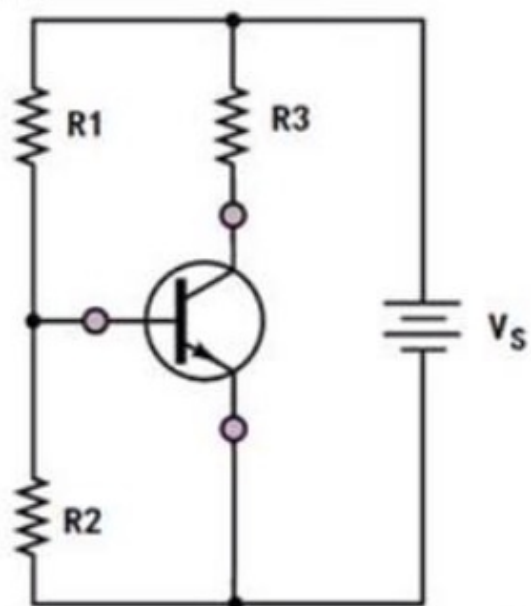Question 2 of 5 


Given the circuit of the figure, determine the base current I_{BQ} and collect voltage V_{CEQ} . Assume a 0.6 V offset voltage, $\beta = 50$, and $V_S = 5$ V.



Given $R_1=100$ k Ω , $R_2=200$ k Ω , and $R_3=500\Omega$.

- ☐ $I_{BQ}=0.032$ mA, $V_{CEQ}= 3.350$ V.
- ☒ $I_{BQ}=0.041$ mA, $V_{CEQ}= 3.975$ V.
- ☐ $I_{BQ}=0.041$ mA, $V_{CEQ}= 3.350$ V.

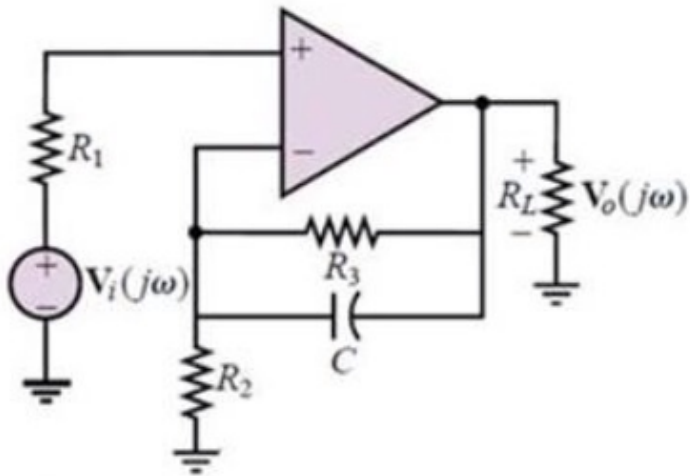The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_V) of the filter.



Given $R_1=2\text{k}\Omega$, $R_2=5\text{k}\Omega$, $R_3=50\text{k}\Omega$, $C=100\text{nF}$.


- ☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_V = 8.22 \text{ dB}$.
- ☒ $\omega_0 = 200 \text{ rad/sec}$; $A_V = 20.83 \text{ dB}$.
- ☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_V = 20.83 \text{ dB}$.
- ☐ $\omega_0 = 200 \text{ rad/sec}$; $A_V = 8.22 \text{ dB}$.

Question 1

20 points

✓ Saved

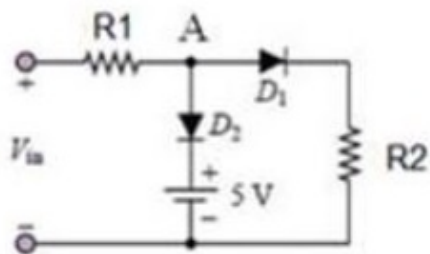Two ideal diodes are connected in a circuit shown in the figure. Calculate the voltage range of V_{in} so that D_1 is "ON" but D_2 is "OFF".



Given $R1 = 9 \text{ k}\Omega$ and $R2 = 12 \text{ k}\Omega$.

- ☐ $0 < V_{in} < 7.75 \text{ V}$
- ☒ $0 < V_{in} < 8.75 \text{ V}$
- ☐ $0 < V_{in} < 7.25 \text{ V}$
- ☐ $0 < V_{in} < 8.25 \text{ V}$




Moving to the next question prevents changes to this answer.

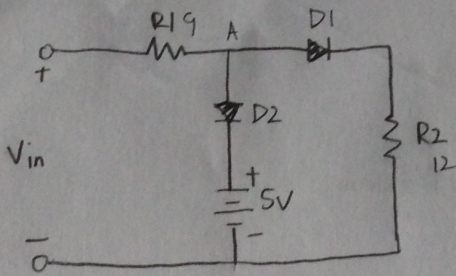Question 1 of 5 >


MA2009 Quiz 2

- Calculate V_{in} so that $D_1 = ON$ $D_2 = OFF$



Given $R_1 = 9k\Omega$ $R_2 = 12k\Omega$


$\rightarrow 0 < V_{in} < 8.75V$

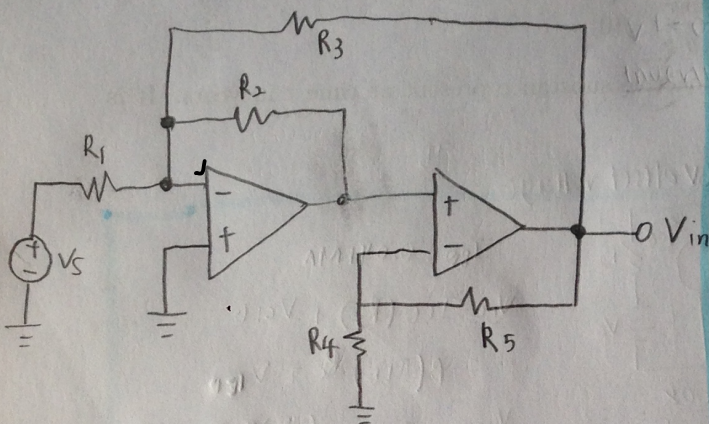

$R_1 = 10\Omega$, $R_2 = 10\Omega$, $R_3 = 10\Omega$, $R_4 = 10\Omega$, $R_5 = 30\Omega$

$\rightarrow A_v = -0.8 \left(\frac{V}{V}\right)$

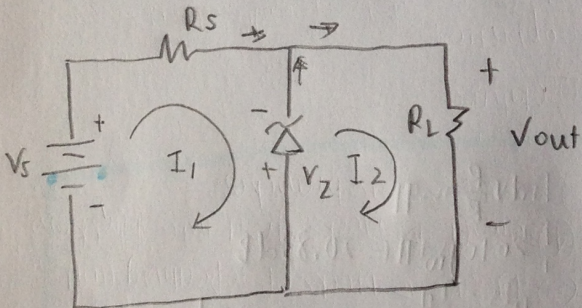- Find minimum value of R_L for which $V_{out} = V_Z$



$V_s = 25V$, $V_Z = 15V$, $R_s = 25k\Omega$

$\rightarrow 37.5k\Omega$

$V_{in} > 0$; D_1 will be ON regardless of D_2
 $V_A < 5A$, D_2 is OFF

$$I_{D1} = \frac{V_{in}}{R_1}$$

$$V_{D1} = \frac{12}{12+9} (V_{in})$$

$$V_{in} = \frac{12}{12+9} \div 5 = 8.75V$$

Non-inverting

$$V^+ = 0$$

Inverting

$$V^- = V^+ = 0$$

$$-I_f = I_t$$

$$-\left(\frac{V_s - V^-}{R_1}\right) = \frac{V_B^+}{R_2} + \frac{V_{out} - V^-}{R_3}$$

$$-\frac{V_s}{R_1} = \frac{V_{out}}{R_3} + \frac{V_B^+}{R_2}$$

$$V_B^+ = \left[-\frac{V_s}{R_1} - \frac{V_{out}}{R_3}\right] R_2$$

Inverting

$$I_{in} = I_f + I_s$$

$$-I_s = -I_f$$

$$\frac{V_B^-}{R_4} = -\left(\frac{V_B^- - V_{out}}{R_5}\right)$$

$$\frac{V_B^-}{R_4} = \frac{V_{out} - V_B^-}{R_5}$$

$$V_B^- \left(\frac{1}{R_4} + \frac{1}{R_5}\right) = \frac{V_{out}}{R_5}$$

$$V_B^- = V_B^+ = \frac{V_{out}}{R_5} \left(\frac{R_4 R_5}{R_4 + R_5}\right)$$

$$V_B^+ = V_{out} \left[\frac{R_4}{R_4 + R_5}\right]$$

$$-\frac{V_s}{R_1} = \frac{V_{out}}{R_3} + V_{out} \left[\frac{R_4}{R_2(R_4 + R_5)}\right]$$

$$-\frac{1}{10} V_s = \frac{1}{10} V_{out} + \frac{1}{40} V_{out}$$

$$-\frac{1}{10} V_s = -\frac{1}{8} V_{out}$$

$$\frac{V_{out}}{V_s} = -0.8$$

$$I_1 = \frac{25-15}{25000} = 0.0004$$

$$I_2 = \frac{15}{R_L}$$

$$I_Z = I_1 - I_2$$

$$= 0.0004 - \frac{15}{R_L} \geq 0$$

$$-\frac{15}{R_L} \geq -0.0004$$

$$\frac{15}{R_L} \leq 0.0004$$

$$15 \leq 0.0004 R_L$$



$$R_L \geq \frac{15}{0.0004} = 37500 \Omega$$

Diode must be ON

$$V = 0$$

$$I > 0$$

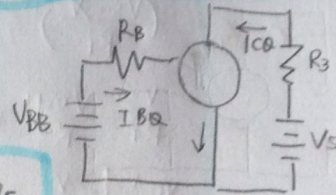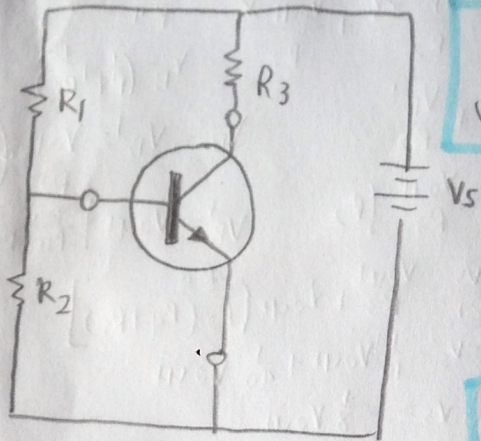- Determine base current $I_{BQ} \approx V_{CEQ}$. Assume 0.6V offset voltage



$$I_{BQ} = 0.041 \text{ mA}$$

$$V_S = I_{CQ}(R_3) + V_{CEQ}$$

$$= \beta(I_{BQ})R_C + V_{CEQ}$$

$$V_{CEQ} = 5 - 50(0.041 \text{ mA})(500 \Omega) = 3.975 \text{ V}$$

$$V_{BB} = \frac{5 \cdot 200 \text{ k}}{(200 + 100) \text{ k}} = 3.33$$

$$R_B = \left(\frac{1}{200} + \frac{1}{100} \right)^{-1} = 66.67 \text{ k}\Omega$$


$$V_{BB} = I_{BQ}(R_B) + V_{BEQ} \rightarrow 0.6$$

$$3.33 = I_{BQ}(66.67 \text{ k}) + 0.6$$

$$\beta = 50, V_S = 5 \text{ V}, R_1 = 100 \text{ k}\Omega, R_2 = 200 \text{ k}\Omega, R_3 = 500 \Omega$$

$$\rightarrow I_{BQ} = 0.041 \text{ mA}, V_{CEQ} = 3.975 \text{ V}$$

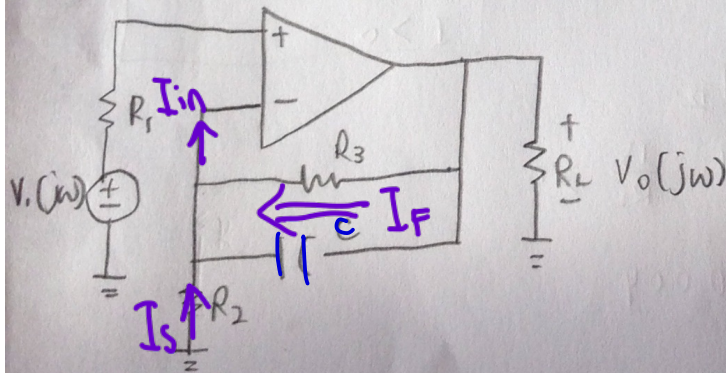- Determine cutoff freq (ω_0) & pass band gain (A_v)



Non-inverting

$$V^+ = V_i(j\omega)$$

Inverting

$$V^+ = V^-$$

$$I_{in} = I_s + I_f$$

$$-I_s = I_f$$

$$-\left[\frac{0 - V_{in}}{R_2} \right] = \left[\frac{V_o - V_{in}}{R_3 \parallel C} \right]$$

$$\frac{V_{in}}{R_2} = V_o - V_{in} \left[\frac{1 + j\omega C R_3}{R_3} \right]$$

$$\frac{V_o - V_{in}}{V_{in}} = \frac{R_3}{R_2} \left[\frac{1}{1 + j\omega C R_3} \right]$$

$$\frac{V_o}{V_{in}} = \underbrace{1 + \frac{R_3}{R_2}}_{\text{gain}} \left[\frac{1}{1 + j\omega C R_3} \right] \leftarrow \text{bandwidth}$$

$$\left| 1 + \frac{R_3}{R_2} \right| = 11 = A$$

$$20 \log_{10} 11 = 20.83 \text{ dB}$$

$$\omega_0 = \frac{1}{C R_3} = 200 \text{ rad/s}$$


$$R_3 \parallel C = \left\{ \frac{1}{R_3} + \left[\frac{1}{j\omega C} \right]^{-1} \right\}^{-1}$$

$$= \left[\frac{1}{R_3} + j\omega C \right]^{-1}$$

$$= \frac{R_3}{1 + j\omega C R_3}$$

$$R_1 = 2 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = 50 \text{ k}\Omega, C = 100 \text{ nF}$$
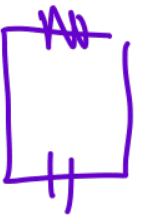
$$\rightarrow \omega_0 = 200 \text{ rad/sec}, A_v = 20.83 \text{ dB}$$



$$\frac{V_{in}}{R_2} = \frac{V_o - V_{in}}{R_3 \parallel C}$$

$$\frac{V_o - V_{in}}{V_{in}} = \frac{1}{R_2} (R_3 \parallel C)$$

$$= \frac{1}{R_2} \left(\frac{R_3}{1 + j\omega C R_3} \right)$$

$$\frac{V_o}{V_{in}} = 1 + \frac{R_3}{R_2} \left(\frac{1}{1 + j\omega C R_3} \right)$$

$$= 1 + \frac{50}{5} \left(\frac{1}{1 + j\omega (100 \times 10^{-9}) (50 \times 10^3)} \right)$$

$$= 1 + 10 \left(\frac{1}{1 + j\omega \frac{1}{200}} \right)$$

$$= 1 + \frac{10}{1 + j\omega \frac{1}{200}}$$

$$= 1 + \frac{2000}{200 + j\omega}$$

$$= \frac{2200 + j\omega}{200 + j\omega}$$

$$20 \log_{10} \sqrt{\frac{2200^2 + \omega^2}{200^2 + \omega^2}}$$

$$= 20 \log_{10} \sqrt{\frac{2200^2 + 200^2}{200^2 + 200^2}}$$

=

$$R_3 \parallel C$$

$$= \left(\frac{1}{R_3} + j\omega C \right)^{-1}$$

$$= \left(\frac{1 + R_3 j\omega C}{R_3} \right)^{-1}$$

$$= \frac{R_3}{1 + R_3 j\omega C}$$

$$R_3 \parallel C$$

$$= \left(\frac{1}{R_3} + \frac{j\omega C}{1} \right)^{-1}$$

$$= \left(\frac{1 + j\omega C R_3}{R_3} \right)^{-1} \quad \frac{1}{j\omega C}$$

$$= \frac{R_3}{1 + j\omega C R_3}$$

gain

$$1 + \frac{50}{10}$$

$$= 11$$

$$\frac{1}{RC} = 200$$

$$\frac{V_{out}}{V_s}(j\omega) = 1 + \frac{Z_F}{Z_S}$$

$$= 1 + \frac{R_3 \parallel C}{R_2}$$

$$= 1 + \frac{1}{R_2} \left(\frac{R_3}{1 + R_3 j\omega C} \right)$$

$$= 1 + \frac{50}{5} \left(\frac{1}{1 + j\omega (50 \times 10^3) (100 \times 10^{-9})} \right)$$

$$= 1 + 10 \left(\frac{1}{1 + j\omega \left(\frac{1}{200} \right)} \right)$$