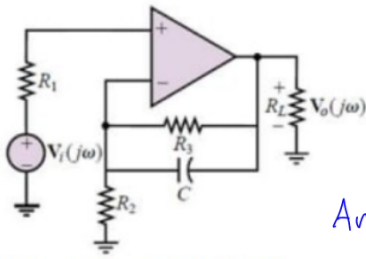


Question 1

30 out of 30 points

The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_V) of the filter.



Given $R_1=2k\Omega$, $R_2=5k\Omega$, $R_3=10k\Omega$, $C=300nF$.

Ans: 9.54

$$V_i = V^+$$

$$\frac{0 - V^-}{R_2} = \frac{V^- - V_o}{R_3}$$

$$-\frac{V_i}{R_2} = \frac{V_i - V_o}{R_3}$$

$$-\frac{R_3}{R_2} = \frac{V_i - V_o}{V_i}$$

$$\frac{V_o}{V_i} = \frac{R_3}{R_2} + 1$$

$$|H(j\omega)| = \left| \frac{10k}{5k} + 1 \right|$$


$$= 3$$

$$20 \log_{10} 3 = 9.54 //$$

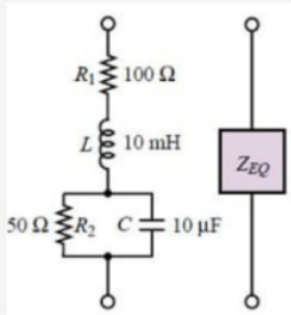Question 2

20 out of 20 points

Which of the following impedances best approximates the equivalent impedance of the following circuit, at frequency $\omega=10^4$ rad/sec?



Ans: $100 + j90\Omega$

$$\frac{1}{Z} = \frac{1}{R_2} + \frac{1}{j\omega C}$$

$$= \frac{1}{R_2} + j\omega C$$


$$Z = \frac{1}{\frac{1}{R_2} + j\omega C} \times R_2$$

$$= \frac{R_2}{1 + j\omega C R_2}$$

$$Z_{EQ} = R_1 + j\omega L + \frac{R_2}{1 + j\omega C R_2}$$

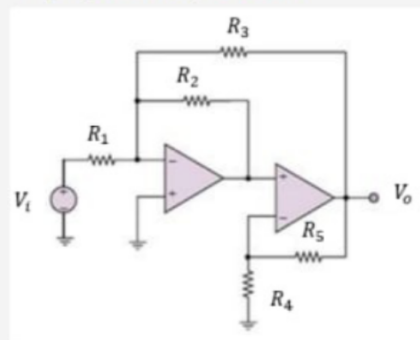Question 3

The op-amps in the following circuit are ideal.



Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=20\Omega$, $R_5=10\Omega$, determine the overall voltage gain $A_V = V_o / V_i$

Ans: -0.6

$$\frac{V_o}{V_i} = -\frac{10(10)(20+10)}{10(20 \times 10 + 10(20+10))}$$

$$\frac{V_i - V}{R_1} = \frac{V - V}{R_2} + \frac{V - V_o}{R_3}$$

$$V_i R_2 R_3 - V R_2 R_3 = V R_1 R_3 - V R_1 R_3 + V R_2 R_1 - V_o R_2 R_1$$

$$V_i R_2 R_3 = -V R_1 R_3 - V_o R_2 R_1$$

$$= -\left(\frac{R_1}{R_4 + R_5}\right) V_o R_1 R_3 - V_o R_2 R_1$$

$$= \left(-\frac{R_1 R_1 R_3}{R_4 + R_5} - R_2 R_1\right) V_o$$

$$\frac{V_o}{V_i} = R_2 R_3 \div \left(-\frac{R_1 R_1 R_3}{R_4 + R_5} - R_2 R_1\right)$$

$$= R_2 R_3 \div \left(-\frac{R_1 R_1 R_3 + R_2 R_1 (R_4 + R_5)}{R_4 + R_5}\right)$$

$$= -\frac{R_2 R_3 (R_4 + R_5)}{R_1 (R_1 R_3 + R_2 (R_4 + R_5))}$$

$$\frac{0 - V}{R_4} = \frac{V - V_o}{R_5}$$

$$-\frac{V}{R_4} = \frac{V - V_o}{R_5}$$

$$-\frac{V}{R_4} = \frac{V}{R_5} - \frac{V_o}{R_5}$$

$$\frac{V}{R_5} + \frac{V}{R_4} = \frac{V_o}{R_5}$$

$$V \left(\frac{1}{R_5} + \frac{1}{R_4}\right) = \frac{R_4 + R_5}{R_5 R_4} V_o$$

$$V = \frac{V_o}{R_5} \div \left(\frac{1}{R_5} + \frac{1}{R_4}\right)$$

$$= \frac{V_o}{R_5} \times \frac{R_4 R_5}{R_4 + R_5}$$

$$= \frac{R_4}{R_4 + R_5} V_o$$

Question 4


Evaluate $(5 + 4j) * (5 - 4j)$ where j is the unitary imaginary number.

Ans: 41

Question 5

10 out of 10 points

Capacitors in series/parallel.

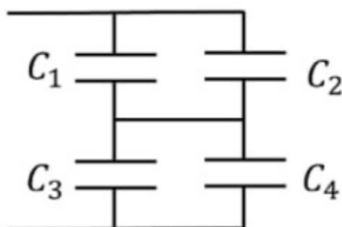


$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{30}$$


$$C_{eq} = 12 \text{ mF} //$$

With reference to the figure, determine the equivalent capacitance when $C_1 = 4 \text{ mF}$, $C_2 = 16 \text{ mF}$, $C_3 = 5 \text{ mF}$, $C_4 = 25 \text{ mF}$.

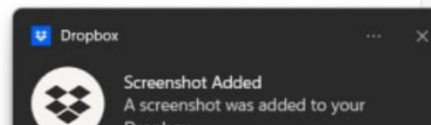Wednesday, November 9, 2022 10:42:30 AM SGT



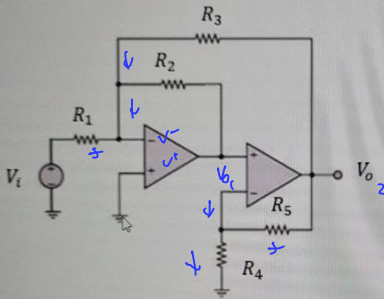The op-amps in the following circuit are ideal.



Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=20\Omega$, $R_5=10\Omega$, determine the overall voltage gain $A_V=V_{o2}/V_i$

- ☐ a. $A_V = +0.6$
- ☐ b. $A_V = +1.5$
- ☐ c. $A_V = -0.6$
- ☐ d. $A_V = -1.5$

$$i_1 + i_2 + i_3 = i_{in} = 0$$

$$\frac{V_s - V^-}{R_1} + \frac{V_{o1} - V^-}{R_2} + \frac{V_{o2} - V^-}{R_3} = 0$$

$$V^+ = V^- = 0$$

$$\frac{V_s}{R_1} + \frac{V_{o1}}{R_3} = -\frac{V_{o1}}{R_2}$$

$$-R_2 \left(\frac{V_s}{R_1} + \frac{V_{o1}}{R_3} \right) = V_{o1} \quad (1)$$

Sub (1) into (2)

$$-R_2 \left(\frac{V_s}{R_1} + \frac{V_{o1}}{R_3} \right) = V_{o1} \left(\frac{R_4}{R_5 + R_4} \right)$$

$$\frac{V_s}{R_1} + \frac{V_{o1}}{R_3} = V_{o1} \left(\frac{R_4}{(R_5 + R_4)(-R_2)} \right)$$

$$\frac{V_s}{10} + \frac{V_{o1}}{10} = -\frac{V_{o1}}{15}$$

$$\frac{V_s}{10} = \frac{V_{o1}}{6}$$

$$i_{in} = i_5 + i_4$$

$$\frac{V^-}{R_4} = -\frac{(V^- - V_{o2})}{R_5}$$

$$V^- = V^+ = V_{o1}$$

$$V_{o1} \left(\frac{1}{R_5} + \frac{1}{R_4} \right) = \frac{V_{o2}}{R_5}$$

$$V_{o1} = \frac{V_{o2}}{R_5} \left(\frac{R_4 R_5}{R_5 + R_4} \right) \quad (2)$$

$$\frac{V_{o2}}{V_s} = -\frac{6}{10} = -0.6$$

$$V_2^- = \frac{V_o}{R_5 + R_4}$$

$$\begin{aligned}\therefore V_2^- &= \frac{R_4}{R_5 + R_4} V_o \\ &= \frac{20}{10 + 20} V_o \\ &= \frac{2}{3} V_o\end{aligned}$$

$$V_2^+ = V_2^- = \frac{2}{3} V_o$$

$$V_i^+ = V_i^- = 0$$

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_i - V_i^-}{R_1} + \frac{V_2^+}{R_2} + \frac{V_o}{R_3} = 0$$


$$\frac{V_i}{10} + \frac{2}{3} V_o \left(\frac{1}{10} \right) + \frac{V_o}{10} = 0$$

$$\frac{V_i}{10} + \frac{V_o}{6} = 0$$

$$\begin{aligned}\frac{V_o}{V_i} &= -\frac{6}{10} \\ &= -0.6\end{aligned}$$

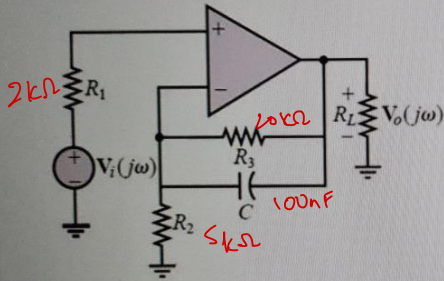
Question 3

The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_V) of the filter.



Given $R_1 = 2k\Omega$, $R_2 = 5k\Omega$, $R_3 = 20k\Omega$, $C = 100nF$.

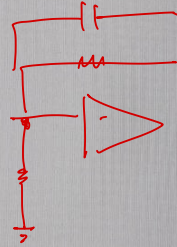- ☒ $\omega_0 = 500$ rad/sec; $A_V = 13.98$ dB.
☐ $\omega_0 = 500$ rad/sec; $A_V = 8.22$ dB.
☐ $\omega_0 = 2000$ rad/sec; $A_V = 8.22$ dB.
☐ $\omega_0 = 2000$ rad/sec; $A_V = 13.98$ dB.



Look @ non inverting amp

$$A_{HP} = 1 + \frac{Z_F}{Z_S}$$

$$Z_F = R_3 \parallel \frac{1}{j\omega C} = \frac{R_3}{1 + j\omega C R_3}$$

$$Z_S = R_2$$

$$A_{HP} = 1 + \frac{R_3}{R_2} \cdot \frac{1}{1 + j\omega C R_3}$$


$$|A_{HP}| = 1 + \frac{20}{5} \cdot \frac{1}{\sqrt{1 + \omega^2 C^2 R_3^2}} \quad \begin{matrix} \nearrow \omega = 0 \rightarrow 5 = 20 \log 5 = 13.98 \text{ dB} \\ \searrow \omega = \infty \rightarrow 0 \end{matrix}$$

$$\begin{aligned} \omega_0 &= \frac{1}{C R_3} \\ &= \frac{1}{1 \times 10^{-7} \times 20 \times 10^3} \\ &= 500 \text{ rad/sec} \end{aligned}$$

⚠ Moving to the next question prevents changes to this answer.

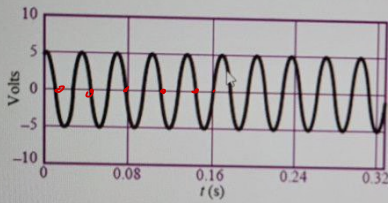Question 2

The following figure represents a sinusoidal voltage in a Voltage vs. Time graph, where time is expressed in second.



Which of the following options best represents the frequency of the following sinusoidal signal?

- ☐ a. 30 Hz
- ☐ b. 3.10 Hz
- ☐ c. 0.32 Hz
- ☐ d. 12.5 Hz

⚠ Moving to the next question prevents changes to this answer.

$$f = \frac{1}{T} = \frac{1}{0.0032}$$


$$= 31.25$$

$$\approx 30 \text{ Hz}$$

$$\frac{0.08}{2.5} = 0.032$$

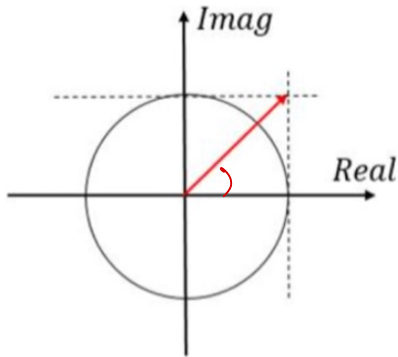Question 3

The figure below represents the complex plane and, in it, a vector (arrow) and the unitary circle.



Which of the following complex numbers best represents the vector?

- ☒ a. $e^{j\pi/4}$
- ☐ b. $\sqrt{2}e^{j\pi/4}$
- ☐ c. $\sqrt{2}e^{j\pi}$
- ☐ d. $\sqrt{2}$

$$\pi = 180^\circ$$


$$45^\circ = \frac{\pi}{4} \Rightarrow e^{j\pi/4}$$

$$e^{j\theta} = \cos\theta + j\sin\theta \\ = \frac{1}{\sqrt{2}} + \frac{j}{\sqrt{2}}$$

$$Re + Im = a \angle \theta$$

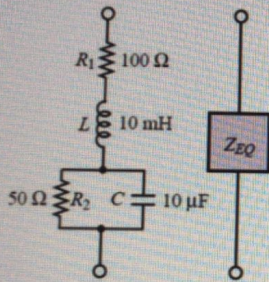Question 4

Which of the following impedances best approximates the equivalent impedance of the following circuit, at frequency $\omega = 10^4 \text{ rad/sec}$?



- ☐ a. $Z_{EQ} = j100 \Omega$
- ☒ b. $Z_{EQ} = 100 + j90 \Omega$
- ☐ c. $Z_{EQ} = 100 e^{j\pi/2} \Omega$
- ☐ d. $Z_{EQ} = 100 + 100 e^{j\pi} \Omega$

$$\omega = 10^4 \text{ rad/sec}$$

$$(a+b)(a-b) = a^2 - b^2$$

$$Z_{eq} = R_1 + L + C // R_2$$

$$= 100 + j\omega L + \left(\frac{1}{R_2} + \frac{1}{\frac{1}{j\omega C}} \right)^{-1}$$