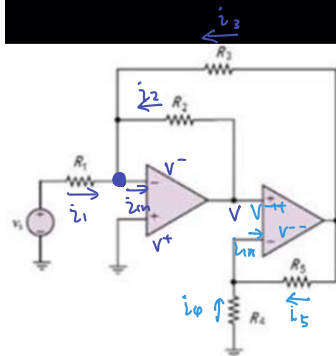




$$i_1 + i_2 + i_3 = i_{IN} = 0$$

$$\frac{V_1 - V^-}{R_1} + \frac{V - V^-}{R_2} + \frac{V_0 - V^-}{R_3} = 0$$

$$V^+ = V^- = 0$$

$$\frac{V_1}{R_1} + \frac{V}{R_2} + \frac{V_0}{R_3} = 0 \quad \left| \quad \frac{V_1}{10} + \frac{V}{10} + \frac{V_0}{10} = 0 \right| \quad V = -V_0 - V_1$$

Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=30\Omega$.

☐ $A_v = -2.25(V/V)$

☐ $A_v = 0.80(V/V)$

☒ $A_v = -0.80(V/V)$ //

☐ $A_v = 2.25(V/V)$

$$\frac{V}{10} + \frac{V}{30} = \frac{V_0}{30}$$

Input Values

R1	10
R2	10
R3	10
R4	10
R5	30
Vout	-1
Vin	1.25
Av	-0.8


$$\frac{V_0}{V_i} = - \frac{10 \times 10 (10 + 30)}{10 (10 \times 10 + 10 (10 + 30))}$$

$$= - \frac{4}{5}$$

$$= -0.8$$

//

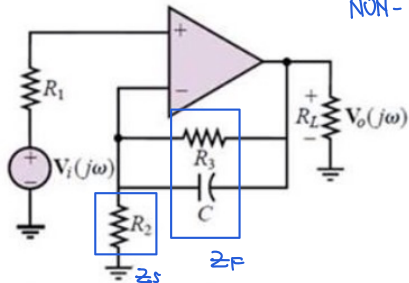The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_v) of the filter.



NON - INVERTING

$$A_v = 20 \log \left(1 + \frac{50}{5} \right)$$

$$= 20.827 \text{ dB}$$

$$\omega_0 = \frac{1}{R_3 \cdot C}$$

$$= \frac{1}{(50000)(100 \times 10^{-9})} \approx 200 \text{ rad/s}$$

Given $R_1=2\text{k}\Omega$, $R_2=5\text{k}\Omega$, $R_3=50\text{k}\Omega$, $C=100\text{nF}$.


- ☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$.
☒ $\omega_0 = 200 \text{ rad/sec}$; $A_v = 20.83 \text{ dB}$.
☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_v = 20.83 \text{ dB}$.
☐ $\omega_0 = 200 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$.

Input

R1	2			
R2	5			
R3	50		SI unit (R3, kilo)	5.00E+04
C	100.00		SI Unit C, Nano	0
Wo	200.00	rad/s		
Vout/vin	11			
Gain (DB)	20.827854			


Question 3

Referring to the following circuit

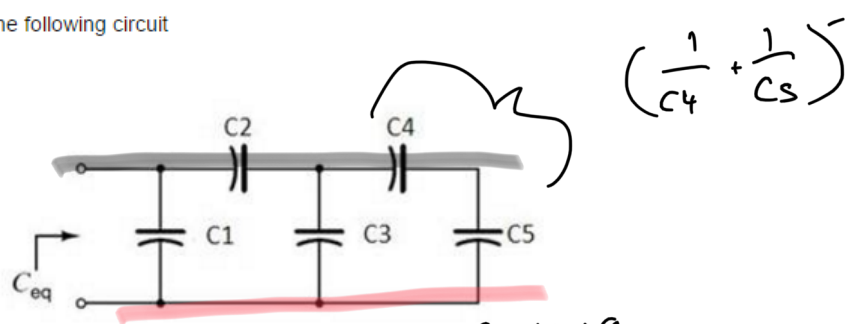

and knowing that

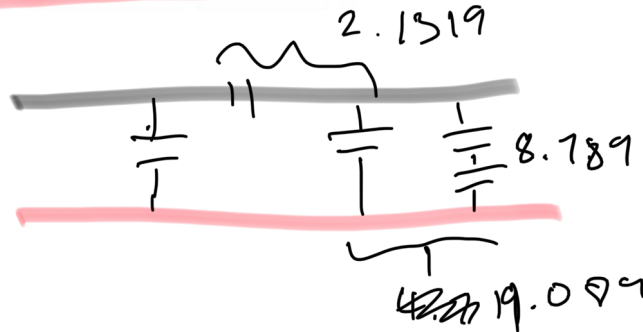C1 = 1.5 [uF]
C2 = 2.4 [uF]
C3 = 10.3 [uF]
C4 = 20.3 [uF]
C5 = 15.5 [uF]



determine the value of the equivalent capacitor C_{eq} (NOTE: uF stands for micro-Farad).

Allowing for some numerical approximation, which among the following values most closely matches the correct answer?

- ☒ $C_{eq} = 3.632$ [uF]
- ☐ $C_{eq} = 22.7274$ [uF]
- ☐ $C_{eq} = 10.8959$ [uF]
- ☐ $C_{eq} = 50$ [uF]

$$\text{series: } \left(\frac{1}{C_4} + \frac{1}{C_5} \right)^{-1} = \left(\frac{1}{20.3} + \frac{1}{15.5} \right)^{-1} = 2.1319$$

$$= 8.789$$

$$\text{Parallel: } 8.789 + 10.3 = 19.089$$

$$2.1319 + 1.5 = 3.6319$$

Answer: C_{eq}


3.631957

[Handwritten signature]

capacitor open
inductor short

Question 5

Referring to the following circuit

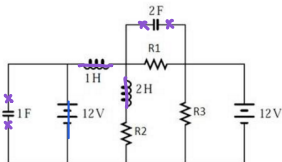

$$W_L = \frac{1}{2} L i_L^2$$

$$W_C = \frac{1}{2} C V_C^2$$

and knowing that

R1 = 13.8 [Ohms]
R2 = 27.6 [Ohms]
R3 = 13.8 [Ohms]

determine the total energy E stored in the circuit at steady state.

Allowing for some numerical approximation, which among the following values most closely matches the correct answer?

[Hint: there is no need to solve any complex system of equations, just a few simple calculations. Look carefully at the circuit!!!!]

- ☐ E = 331.2 J
- ☒ E = 72.2836 J
- ☐ E = 0 J
- ☐ E = 243.36 J

After Steady State

R1	13.8
R2	27.6
R3	13.8
Voltage	12

Mesh Current 1

i1	27.6
i2	-27.6
i3	0
Voltage	12

Mesh Current 2

i1	-27.6
i2	55.2
i3	-13.8
Volatge	0

Mesh Current 3

i1	0
i2	-13.8
i3	13.8
Volatge	-12

After Solving Simultaneous Equation


i1	6.0000
i2	0.0000
i3	-12.0000

Energy

1F	1.0000	72
2F	2.0000	0
1H	1.0000	18
2H	2.0000	36

Asnwer: Total Energy 126
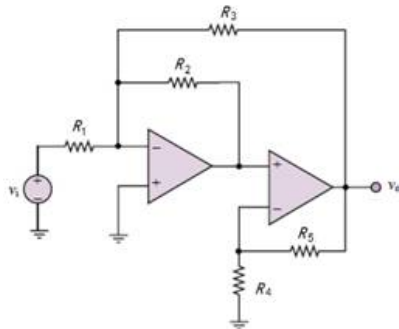
$$A = \begin{bmatrix} 27.6 & -27.6 & 0 \\ -27.6 & 55.2 & -13.8 \\ 0 & -13.8 & 13.8 \end{bmatrix} \quad X = \begin{bmatrix} i1 \\ i2 \\ i3 \end{bmatrix} \quad B = \begin{bmatrix} 12 \\ 0 \\ -12 \end{bmatrix}$$



$$\frac{V_o}{V_i} = -$$

Given $R_1=30\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=10\Omega$.

Selected Answer: ☒ $A_v = -0.22$ (V/V)

Answers: $A_v = -1.78$ (V/V)

$A_v = 0.22$ (V/V)

☒ $A_v = -0.22$ (V/V)

$A_v = 1.78$ (V/V)


25 out of 25 points

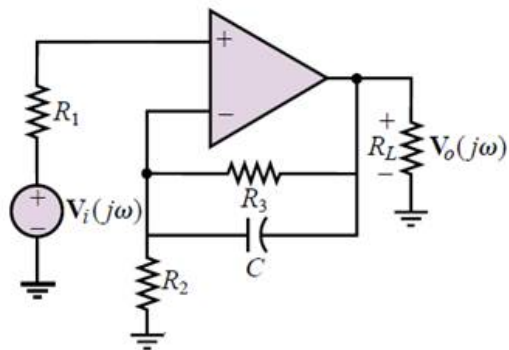Question 4

25 out of 25 points



The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_V) of the filter.



Given $R_1=2\text{k}\Omega$, $R_2=5\text{k}\Omega$, $R_3=40\text{k}\Omega$, $C=100\text{nF}$.

Selected Answer: ☒ $\omega_0 = 250 \text{ rad/sec}$; $A_V = 19.08 \text{ dB}$.

Answers: ☒ $\omega_0 = 250 \text{ rad/sec}$; $A_V = 19.08 \text{ dB}$.

$\omega_0 = 2000 \text{ rad/sec}$; $A_V = 19.08 \text{ dB}$.

$\omega_0 = 2000 \text{ rad/sec}$; $A_V = 8.22 \text{ dB}$.


$\omega_0 = 250 \text{ rad/sec}$; $A_V = 8.22 \text{ dB}$.

Wednesday, November 13, 2019 11:08:46 AM SGT

← OK

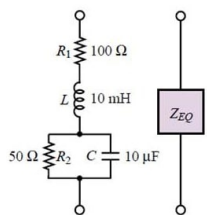
Question 4

Which of the following impedances best approximates the equivalent impedance of the following circuit, at frequency $\omega = 10^4$ rad/sec?



- ☐ a. $Z_{EQ} = 100 + 100 e^{j\pi}\ \Omega$
- ☒ b. $Z_{EQ} = 100 + j90\ \Omega$
- ☐ c. $Z_{EQ} = j100\ \Omega$
- ☐ d. $Z_{EQ} = 100 e^{j\pi/2}\ \Omega$

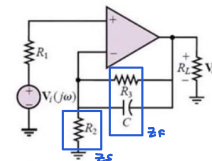The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_v) of the filter.



- Given $R_1=2k\Omega$, $R_2=5k\Omega$, $R_3=50k\Omega$, $C=100nF$.
- ☐ $\omega_0 = 2000$ rad/sec; $A_v = 8.22$ dB
 - ☒ $\omega_0 = 200$ rad/sec; $A_v = 20.83$ dB
 - ☐ $\omega_0 = 2000$ rad/sec; $A_v = 20.83$ dB
 - ☐ $\omega_0 = 200$ rad/sec; $A_v = 8.22$ dB

NON INVERTING

$$Z_F = R/C$$

$$= \left(\frac{1}{R_3} + j\omega C \right)^{-1}$$

$$= \left(\frac{1 + R_3 j\omega C}{R_3} \right)^{-1}$$

$$= \frac{R_3}{1 + j\omega C R_3}$$

$$Z_S = R_2$$

$$A_v = \frac{V_o}{V_i} = 1 + \frac{Z_F}{Z_S} = \frac{R_2}{R_2} \left(\frac{1}{1 + R_3 j\omega C} \right)$$

low pass

$$\omega \rightarrow 0 \Rightarrow 1$$

$$\omega \rightarrow \infty \Rightarrow 0$$

$$A_v(j\omega) = 1 + \frac{R_2}{R_2} (1) \text{ where } \omega \rightarrow 0$$

$$= 1 + \frac{50}{5}$$

$$= 11$$


$$\text{gain} = 20 \log_{10} 11 = 20.83 \text{ dB}$$

$$\omega_0 = \frac{1}{R_3 C} = \frac{1}{50000 \times 100 \times 10^{-9}}$$

$$= 200 \text{ rad/s}$$

$Z_F :$

167

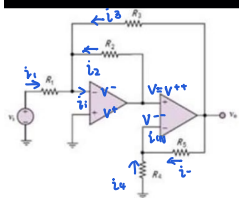

Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=30\Omega$.

- ☐ $A_v = -2.25(V/V)$
☐ $A_v = 0.80(V/V)$
☒ $A_v = -0.80(V/V)$
☐ $A_v = 2.25(V/V)$

$$i_{in} = i_1 + i_2 + i_3 = 0$$

$$\frac{V_i - V^-}{R_1} + \frac{V^- - V^-}{R_2} + \frac{V_0 - V^-}{R_3} = 0$$

$$V^- = V^+ = 0$$

$$\frac{V_i}{R_1} + \frac{V}{R_2} + \frac{V_0}{R_3} = 0$$

$$i_{in} = i_4 + i_5 = 0$$

$$-\frac{V^-}{R_4} + \frac{V_0 - V^-}{R_5} = 0$$

$$V^+ = V^- = V$$

$$-\frac{V}{R_4} + \frac{V_0}{R_5} - \frac{V}{R_5} = 0$$

$$\frac{V}{R_4} + \frac{V}{R_5} = \frac{V_0}{R_5}$$

$$\frac{VR_5 + VR_4}{R_4R_5} = \frac{V_0}{R_5}$$

$$V = \frac{R_4R_5V_0}{R_5(R_4 + R_5)}$$

$$= V_0 \left(\frac{R_4}{R_4 + R_5} \right)$$

$$\frac{V_i}{R_1} + \frac{V_0}{R_2} \left(\frac{R_4}{R_4 + R_5} \right) + \frac{V_0}{R_3} = 0$$

$$\frac{V_i}{10} + \frac{V_0}{10} \left(\frac{10}{10+30} \right) + \frac{V_0}{10} = 0$$

$$V_i + 1.25V_0 = 0$$

$$V_i = -1.25V_0$$

$$\frac{V_0}{V_i} = (-1.25)^{-1} = -0.8$$

Question 5

Write colour

If $V_{in} = 5\angle 20^\circ$ and $V_{out} = 10\angle 45^\circ$, in phasor format (amplitude $\angle$ angle), which of the following phasors best represent the ratio V_{out} / V_{in} ?

☐ $0.5\angle -15^\circ$

☐ $5\angle -15^\circ$

☒ $2\angle 15^\circ$

☐ $15\angle 65^\circ$

$$\frac{10}{5} \angle 45 - 20$$

$$= 2 \angle 15$$


→  Click **Submit** to complete this assessment.

$$4.69 + 1.7j$$

$$7.07 + 9.07j$$

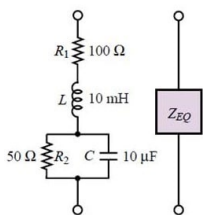Question 4

Which of the following impedances best approximates the equivalent impedance of the following circuit, at frequency $\omega = 10^4$ rad/sec?



- ☐ a. $Z_{EQ} = 100 + 100 e^{j\pi} \Omega$
- ☒ b. $Z_{EQ} = 100 + j90 \Omega$
- ☐ c. $Z_{EQ} = j100 \Omega$
- ☐ d. $Z_{EQ} = 100 e^{j\pi/2} \Omega$

$$\begin{aligned}
 Z_{RC} &= \left(\frac{1}{R} + j\omega C \right)^{-1} \\
 &= \left[\frac{1}{50} + j(10^4 \times 10 \times 10^{-6}) \right]^{-1} \\
 &= (0.02 + 0.1j)^{-1} \\
 &= \frac{1}{0.02 + 0.1j} \times \frac{(0.02 - 0.1j)}{(0.02 - 0.1j)} \\
 &= \frac{0.02 - 0.1j}{0.02^2 + 0.1^2} \\
 &= \frac{0.02}{0.0104} - \frac{0.1}{0.0104} j
 \end{aligned}$$


$$Z_{eq} = \frac{0.02}{0.0104} + 100 - \frac{0.1}{0.0104} j + j(10^4)(10 \times 10^{-3})$$

$$= 101.9 + 90.38 j$$

$$\begin{aligned}
 &100 + j\omega L + \left(\frac{1}{50} + \frac{1}{j\omega C} \right)^{-1} \\
 &100 + j10^4(10 \times 10^{-3}) + \left(\frac{1}{50} + \frac{1}{10^4(10 \times 10^{-6})j} \right)^{-1} \\
 &100 + 100j + \left(\frac{1}{50} + \frac{1}{100j} \right)^{-1} \\
 &100 + 100j + \left(\frac{100j + 50}{5000j} \right)^{-1} \\
 &100 + 100j + \frac{5000j}{100j + 50}
 \end{aligned}$$

Question 3

Capacitors in series/parallel.

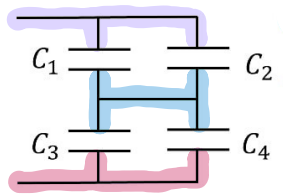

$$C_1 // C_2 + C_3 // C_4$$

$$C_1 // C_2 = 4 + 16 = 20 \text{ mF}$$

$$C_3 // C_4 = 9 + 21 = 30 \text{ mF}$$

$$C_T = \left(\frac{1}{20} + \frac{1}{30} \right)^{-1}$$

$$= 12 \text{ mF}$$

With reference to the figure, determine the equivalent capacitance when $C_1 = 4 \text{ mF}$, $C_2 = 16 \text{ mF}$, $C_3 = 9 \text{ mF}$, $C_4 = 21 \text{ mF}$.

- ☒ Ceq = 12 mF
☐ Ceq = 46 mF
☐ Ceq = 84 mF
☐ Ceq = 29 mF


$$C_1 // C_2 = 13 + 7$$

$$= 20$$

$$C_3 // C_4 = 11 + 19$$

$$= 30$$

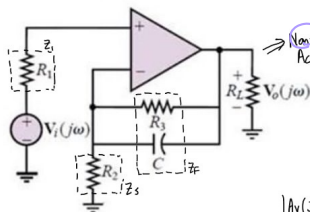The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_0) and pass-band gain (A_v) of the filter.



?? +ve terminal
Non-inverting Active Filter 因为含有 capacitor

$$Z_F = \frac{R_1 \left(\frac{1}{j\omega C} \right)}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{R_1 j\omega C + 1}$$

$$Z_S = R_2$$

$$A_v = \frac{V_o}{V_i} = 1 + \frac{Z_F}{Z_S} = 1 + \frac{R_1}{R_2} \left(\frac{1}{R_1 j\omega C + 1} \right)$$

$$|A_v(j\omega)| = 1 + \frac{R_1}{R_2} (1) \text{ where } \omega \rightarrow 0 \quad \omega_0 = \frac{1}{R_2 C} = \frac{1}{50 \times 10^3 \times 10^{-9}}$$

$$= 11 \quad = 200 \text{ rad/s}$$

$$G_{\text{min}} = \frac{1}{\sqrt{1+1}} = 1, \omega \rightarrow 0 \quad \left. \begin{array}{l} \omega \rightarrow 0 \\ \omega \rightarrow \infty \end{array} \right\} \text{Low pass}$$

Given $R_1=2\text{k}\Omega$, $R_2=5\text{k}\Omega$, $R_3=50\text{k}\Omega$, $C=100\text{nF}$.


☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$.

☒ $\omega_0 = 200 \text{ rad/sec}$; $A_v = 20.83 \text{ dB}$.

☐ $\omega_0 = 2000 \text{ rad/sec}$; $A_v = 20.83 \text{ dB}$.

☐ $\omega_0 = 200 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$.
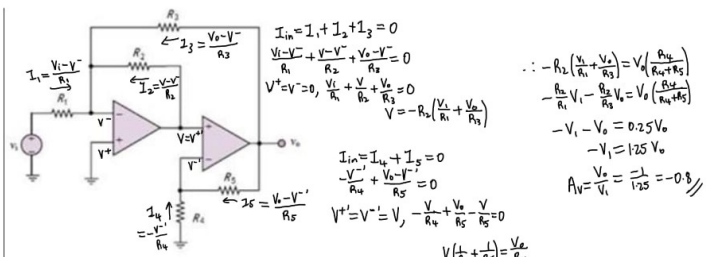
$$G_{\text{min}} = 20 \log_{10}(11) = 20.83 \text{ dB}$$



Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=30\Omega$.

- ☐ $A_V = -2.25(V/V)$
☐ $A_V = 0.80(V/V)$
☒ $A_V = -0.80(V/V)$
☐ $A_V = 2.25(V/V)$

$R_1 = 10$
 $R_2 = 10$
 $R_3 = 10$
 $R_4 = 20$
 $R_5 = 10$


$$-\frac{R_2}{R_1} V_1 - \frac{R_2}{R_3} V_0 = V_0 \left(\frac{R_4}{R_4 + R_5} \right)$$

$$-\frac{10}{10} V_1 - \frac{10}{10} V_0 = V_0 \left(\frac{20}{20 + 10} \right)$$

$$-V_1 - V_0 = \frac{2}{3} V_0$$

$$-V_1 = \frac{5}{3} V_0$$

-0.6

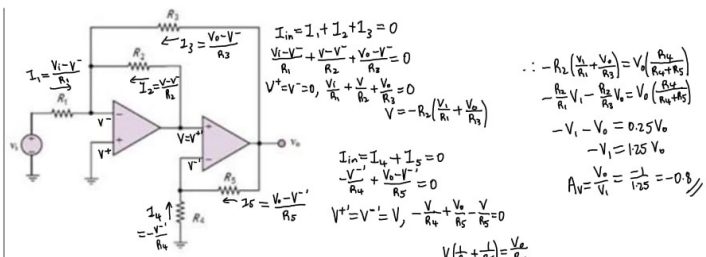

Given $R_1=10\Omega$, $R_2=10\Omega$, $R_3=10\Omega$, $R_4=10\Omega$ and $R_5=30\Omega$.

- ☐ $A_V = -2.25(V/V)$
☐ $A_V = 0.80(V/V)$
☒ $A_V = -0.80(V/V)$
☐ $A_V = 2.25(V/V)$

$R_1 = 10$
 $R_2 = 10$
 $R_3 = 10$
 $R_4 = 20$
 $R_5 = 10$

$$-\frac{R_2}{R_1} V_1 - \frac{R_2}{R_3} V_0 = V_0 \left(\frac{R_4}{R_4 + R_5} \right)$$

$$-\frac{10}{10} V_1 - \frac{10}{10} V_0 = V_0 \left(\frac{20}{20 + 10} \right)$$

$$-V_1 - V_0 = \frac{2}{3} V_0$$

$$-V_1 = \frac{5}{3} V_0$$

-0.6