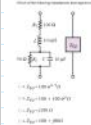


Given $R_1 = 10\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$, $R_4 = 10\text{ k}\Omega$ and $R_5 = 30\text{ k}\Omega$.
 Assume $A_{OL} = 200\text{ V/V}$
 Assume $f_{CL} = 200\text{ kHz}$
 Assume $f_{CU} = 200\text{ kHz}$

Input Values	
R_1	10
R_2	10
R_3	10
R_4	10
R_5	30
V_{DD}	5
V_{SS}	-5
f_{in}	0.159155

Question 1
Which of the following expressions best represents the equivalent impedance of the following circuit, at frequency $\omega = 10^3\text{ rad/s}$?



- ☐ $Z_{eq} = 100 + j10$
- ☐ $Z_{eq} = 100 + j1000$
- ☐ $Z_{eq} = 100 - j1000$
- ☐ $Z_{eq} = 100 - j10$

Question 2
Which of the following expressions best represents the equivalent impedance of the following circuit, at frequency $\omega = 10^3\text{ rad/s}$?



- ☐ $Z_{eq} = 100 + j10$
- ☐ $Z_{eq} = 100 + j1000$
- ☐ $Z_{eq} = 100 - j1000$
- ☐ $Z_{eq} = 100 - j10$

Question 3
Denoting by j the unit imaginary number, which of the following identities is true?



- ☐ $|1 + j|^2 = \sqrt{2}$
- ☐ $j^2 = j$
- ☐ $j + \pi = 0$
- ☐ $1 + e^{j\pi} = 0$

Question 2
The following figure represents a sinusoidal voltage in a voltage vs. Time graph, where time is expressed in seconds.

Which of the following options best represents the frequency of the following sinusoidal signal?

- ☐ $\omega = 30\text{ Hz}$
- ☐ $\omega = 3.14\text{ kHz}$
- ☐ $\omega = 0.314\text{ Hz}$
- ☐ $\omega = 0.314\text{ kHz}$

Question 3
The circuit in the following figure is an active filter. Determine the cutoff frequency (in Hz) and pass band gain (in dB) of the filter.

Given $R_1 = 10\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$, $R_4 = 10\text{ k}\Omega$, $R_5 = 30\text{ k}\Omega$, determine the output voltage gain $A_v = V_o/V_i$.

- ☐ $A_v = 10$
- ☐ $A_v = 10.4$
- ☐ $A_v = 10.8$
- ☐ $A_v = 11$

Question 1
The circuit shown in the figure is an active filter with. Determine the cutoff frequency (in Hz) and pass band gain (in dB) of the filter.

Given $R_1 = 10\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$, $R_4 = 10\text{ k}\Omega$, $R_5 = 30\text{ k}\Omega$, determine the output voltage gain $A_v = V_o/V_i$.

- ☐ $A_v = 10$
- ☐ $A_v = 10.4$
- ☐ $A_v = 10.8$
- ☐ $A_v = 11$

The circuit shown in the figure is an active filter with. Determine the cutoff frequency (in Hz) and pass band gain (in dB) of the filter.

Given $R_1 = 10\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$, $R_4 = 10\text{ k}\Omega$, $R_5 = 30\text{ k}\Omega$, determine the output voltage gain $A_v = V_o/V_i$.

- ☐ $A_v = 10$
- ☐ $A_v = 10.4$
- ☐ $A_v = 10.8$
- ☐ $A_v = 11$

Question 2
The following figure represents a sinusoidal voltage in a voltage vs. Time graph, where time is expressed in seconds.

Which of the following options best represents the frequency of the following sinusoidal signal?

- ☐ $\omega = 30\text{ Hz}$
- ☐ $\omega = 3.14\text{ kHz}$
- ☐ $\omega = 0.314\text{ Hz}$
- ☐ $\omega = 0.314\text{ kHz}$

Question 1
Which of the following expressions best represents the equivalent impedance of the following circuit, at frequency $\omega = 10^3\text{ rad/s}$?

Which of the following expressions best represents the equivalent impedance of the following circuit, at frequency $\omega = 10^3\text{ rad/s}$?

- ☐ $Z_{eq} = 100 + j10$
- ☒ $Z_{eq} = 100 + j1000$
- ☐ $Z_{eq} = 100 - j1000$
- ☐ $Z_{eq} = 100 - j10$

Question 3
Evaluate $(5 + 4j) \cdot (5 - 4j)$ where j is the unitary imaginary number.

- ☒ 41
- ☐ 9
- ☐ $25 + 16j$
- ☐ $25 - 16j$

Total cycles = 9.5 thru 0.325
 $F = \frac{9.5}{0.32}$
 ≈ 29.6875
 $\approx 2\pi$

$\omega = 2\pi f$
 $f = \frac{1}{T}$

$Z_{eq} = R_1 + j\omega L + \frac{R_2}{j\omega C}$
 $= R_1 + j\omega L + \frac{R_2}{j\omega C}$

$Z_s = R_1 + j\omega L$
 $Z_f = \frac{R_2}{1 + j\omega R_1 C}$

$\frac{50}{1 + 5j} \times \frac{1 - 5j}{1 - 5j}$

$(5 + 4j)(5 - 4j)$

Total cycles = 9.5 thru 0.335

$$F = \frac{9.5}{0.32}$$

$$= 29.6875 \approx 30$$

$$W = 2\pi f$$

$$f = \frac{1}{T}$$


$$\begin{aligned} Z_{EQ} &= R_1 + j\omega L + R_2 // \frac{1}{j\omega C} \\ &= R_1 + j\omega L + \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} \\ &= R_1 + j\omega L + \frac{R_2}{1 + j\omega R_2 C} \\ &= (100 + j(10^3)(10 \times 10^{-3})) + \frac{25}{13} - \frac{125}{13}j \\ &= 101.923 + 90.385j \end{aligned}$$

$$Z_S = R_1 + j\omega L$$

$$\begin{aligned} Z_f &= \frac{R_2}{1 + j\omega R_2 C} \\ &= \frac{50}{1 + j(10^3)(50)(10 \times 10^{-6})} = \frac{50 - 250j}{1 - 25j^2} \\ &= \frac{50}{1 + 5j} = \frac{50 - 250j}{1 + 25} = \frac{20}{13} - \frac{125}{13}j \end{aligned}$$

$$\begin{aligned} &(5 + 4j)(5 - 4j) \\ &= 25 - 20j + 20j - 16j^2 \\ &= 25 + 16 \\ &= 41 \end{aligned}$$

Capacitors in series/parallel.

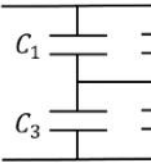

With reference to the figure, determine the

- ☐ Ceq = 42 mF
- ☐ Ceq = 12 mF
- ☐ Ceq = 27 mF
- ☐ Ceq = 184 mF


$$C_1 // C_2 + C_3 // C_4$$

$$= \frac{1}{\frac{1}{C_1 + C_2} + \frac{1}{C_3 + C_4}}$$

$$= \frac{1}{\frac{1}{20} + \frac{1}{30}}$$




$$= 12 \text{ mF}$$

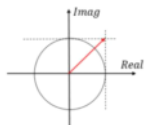The figure below represents the complex plane, a vector



Which of the following complex numbers best represent

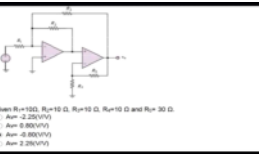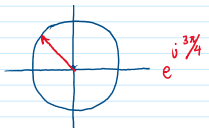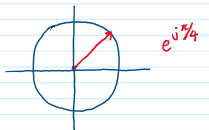- ☒ $\sqrt{2} e^{j\pi/4}$
- ☐ $\sqrt{2}$
- ☐ $2 e^{j\pi/2}$
- ☐ $2 e^{j\pi}$




$$-I_1 - I_2 + I_{in} = 0$$

$$\frac{V_S - V^-}{R_1} + \frac{V_1 - V^-}{R_2} = I_{in}$$

$$\frac{V_S}{R_1} + \frac{V_1}{R_2} + \frac{V_{out}}{R_3} = 0$$

$$V_{O1} = -\frac{V_S}{R_1} - \frac{V_{out}}{R_3}$$
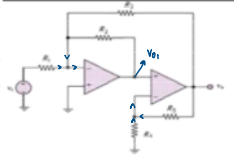
$$V_{O1} = \left(-\frac{V_S}{R_1} - \frac{V_{out}}{R_3} \right) R_2$$



$$-I_4 - I_5 + I_{in2} = 0$$

$$I_4 + I_5 = I_{in2}$$

$$\frac{V_{S2} - V^-}{R_4} + \frac{V_{out} - V^-}{R_5} = I_{in2}$$

$$V_{S2} = 0 \text{ (ground)}$$


$$\frac{0 - (V^-)}{R_4} + \frac{V_{out} - (V^-)}{R_5} = 0$$

$$V_S \frac{R_2}{R_1 R_4} + V_{out} \frac{R_2}{R_3 R_4} + V_{out} \frac{1}{R_5} + V_S \frac{R_2}{R_1 R_5} + V_{out} \frac{R_2}{R_3 R_5} = 0$$

$$V_{out} \left(\frac{1}{R_5} + \frac{R_2}{R_3 R_4} + \frac{R_2}{R_3 R_5} \right) + V_S \left(\frac{R_2}{R_1 R_4} + \frac{R_2}{R_1 R_5} \right) = 0$$

$$V_{out} \left(\frac{1}{6} \right) + V_S \left(\frac{2}{15} \right) = 0$$

$$\frac{V_{out}}{V_S} = -0.8$$

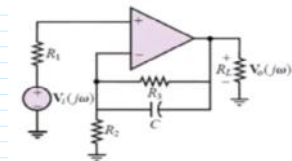

Given $R_1 = 2k\Omega$, $R_2 = 5k\Omega$, $R_3 = 50k\Omega$, $C = 100\mu F$

- ☐ $\omega = 2000 \text{ rad/sec}$, $A_v = 8.22 \text{ dB}$
- ☒ $\omega = 200 \text{ rad/sec}$, $A_v = 20.83 \text{ dB}$
- ☐ $\omega = 2000 \text{ rad/sec}$, $A_v = 20.83 \text{ dB}$
- ☐ $\omega = 200 \text{ rad/sec}$, $A_v = 8.22 \text{ dB}$

Non-inverting

$$H = 1 + \frac{R_2}{R_1}$$

$$Z_S = R_2, \quad Z_f = R_3 // \frac{1}{j\omega C}$$

$$= \frac{R_3 \cdot \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} = \frac{R_3}{1 + R_3 j\omega C}$$

$$H = 1 + \frac{R_3}{1 + R_3 j\omega C}$$

$$\omega \rightarrow 0, H = 1 + \frac{R_3}{R_2}$$

$$= 1 + \frac{R_3}{R_2} = 11$$

$$\omega \rightarrow \infty, H = 1$$

$$\text{Gain} = 20 \log 11$$

$$= 20.83 \text{ dB}$$

$$\omega_0 = \frac{1}{R_3 C}$$

$$= 200 \text{ rad/s}$$

Question 3

Denoting by j the unit imaginary number, which of the following identities is true?

- ☐ $|1 + j^2| = \sqrt{2}$ ☒
- ☐ $j^3 = j$ ☒
- ☐ $j + \pi = 0$
- ☐ $1 + e^{j\pi} = 0$ ☒

$$|1 + (-1)|$$

$$= |0|$$

$$= 0 \neq \sqrt{2}$$

$$j + \pi = 0$$

$$j^3 = j^2 j$$

$$= (-1)j$$

$$= -j \neq j$$

$$e^{j\pi} = -1$$


If $V_{in} = 5 \angle 20^\circ$ and $V_{out} = 10 \angle 45^\circ$, in phasor format (amplitude $\angle$ angle), which of the following phasors best represent the ratio V_{out} / V_{in} ?

- ☐ $0.5 \angle -15^\circ$
- ☐ $15 \angle 65^\circ$
- ☒ $2 \angle 15^\circ$
- ☐ $5 \angle -15^\circ$

$$\frac{V_{out}}{V_{in}} = \frac{10 \angle 45^\circ}{5 \angle 20^\circ}$$

$$= \frac{10}{5} \angle 45 - 20$$

$$= 2 \angle 15^\circ$$

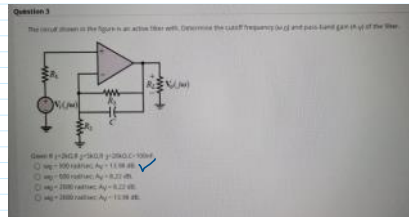

$$H = 1 + \frac{R_3}{R_2} \cdot \frac{1}{1 + j\omega R_3 C}$$

$$\omega \rightarrow 0, H = 1 + \frac{R_3}{R_2}$$

$$= 5$$


$$\omega \rightarrow \infty, H = 1$$

$$\text{Gain} = 20 \log 5$$

$$= 13.98 \text{ dB}$$

$$\omega_0 = \frac{1}{R_3 C}$$


$$= 500 \text{ rad/s}$$

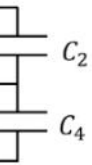

equivalent capacitance when

for (arrow) and the unitary circle.

into the vector?

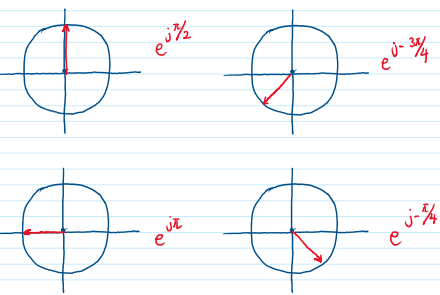

$$= 0 + j2$$

$$= -j \neq j$$

$$= \frac{10}{5} \angle 45 - 20$$

$$= 2 \angle 15^\circ$$

$$j + \pi = 0$$

$$e^{j\pi} = -1$$

HUH?? X

$$e^{j\pi} = \cos \pi + j \sin \pi$$

$$= -1 //$$