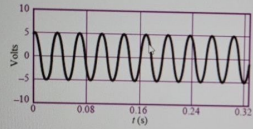


⚠ Moving to the next question prevents changes to this answer.

Question 2

The following figure represents a sinusoidal voltage in a Voltage vs. Time graph, where time is expressed in second.



Which of the following options best represents the frequency of the following sinusoidal signal?

- ☒ a. 30 Hz
- ☐ b. 3.10 Hz
- ☐ c. 0.32 Hz
- ☐ d. 12.5 Hz

2.25 cycles in 0.08 s


⚠ Moving to the next question prevents changes to this answer.

$$t = 0.08 \div 2.25$$
$$= 0.03556$$

$$f = \frac{1}{T} = \frac{1}{0.03556}$$
$$= 28.125 \text{ Hz}$$

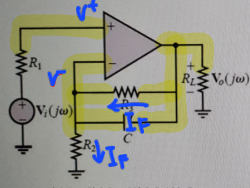Question 3

The circuit shown in the figure is an active filter. Determine the cutoff frequency (ω_0) and pass-band gain (A_v) of the filter.



Given $R_1 = 2k\Omega$, $R_2 = 5k\Omega$, $R_3 = 20k\Omega$, $C = 100nF$.

- ☐ $\omega_0 = 500$ rad/sec; $A_v = 13.98$ dB. ✓
- ☐ $\omega_0 = 500$ rad/sec; $A_v = 8.22$ dB.
- ☐ $\omega_0 = 2000$ rad/sec; $A_v = 8.22$ dB.
- ☐ $\omega_0 = 2000$ rad/sec; $A_v = 13.98$ dB.

$$V^+ = V^- \quad i_{in} = 0 \rightarrow i_s = -i_f$$

$$\frac{V_i - V^+}{R_1} = - \left(\frac{V^- - V_o}{R_2 + \frac{R_3}{1 + j\omega C}} + \frac{V^-}{R_2} \right)$$

$$\frac{V_i - V^-}{R_1} + \frac{V^-}{R_2} = \frac{V_o - V^-}{\left(\frac{R_3}{1 + j\omega C} \right)}$$

$$V_o = \frac{V^-}{R_2} \times \frac{R_3}{1 + j\omega R_3 C} + V^-$$

$$V_i = V^-$$

$$\frac{V_o}{V_i} = \frac{R_3}{R_2 + j\omega R_3 C} + 1$$

$$R_3 \omega = 1$$

$$\omega = \frac{1}{2000 \times 100 \times 10^{-9}} = 500 \text{ rad/s}$$

$$\begin{aligned} \text{gain} &= 5 = \frac{R_3}{R_2} + 1 \\ &= 20 \log_{10} 5 \\ &= 13.98 \text{ dB} \end{aligned}$$



$$V_{in} = V^+ = V^-$$

$$I_F = \frac{V_o - V_i}{R_3 // C} = \frac{V_i}{R_2}$$

$$1 + \frac{Z_F}{Z_S}$$

$$= 1 + \frac{R_3 // C}{R_2}$$

$$\frac{V_o}{//} - \frac{V_i}{//} = \frac{V_i}{R_2}$$

$$\frac{V_o}{//} = \frac{V_i}{R_2} + \frac{V_i}{//}$$

$$\frac{V_o}{V_i} = \left(\frac{1}{R_2} + \frac{1}{//} \right) (//)$$

$$= \frac{//}{R_2} + 1$$

$$= \frac{R_3 // C}{R_2} + 1$$

$$= \frac{R_3}{R_2 (1 + j\omega R_3 C)} + 1$$

$$\omega = \frac{1}{R_3 C}$$

$$\left(\frac{1}{R_3} + j\omega C \right)^{-1}$$

$$= \left(\frac{1 + j\omega C R_3}{R_3} \right)^{-1}$$

=

$$\frac{100 \times 10^3}{20 \times 10^3 (1 + j\omega (100 \times 10^{-9}) (100 \times 10^3))}$$

$$=$$

$$\omega_0 = 100$$


$$20 \log_{10} \left| \frac{R_3}{R_2} + 1 \right|$$

$$= \frac{100}{20} + 1$$

b

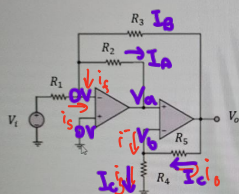15.

The op-amps in the following circuit are ideal.



Given $R_1=100$, $R_2=100$, $R_3=100$, $R_4=200$, $R_5=100$, determine the overall voltage gain $A_V = V_o/V_i$.

- ☐ a. $A_V = -0.6$
- ☐ b. $A_V = +1.5$
- ☒ c. $A_V = -0.6$
- ☐ d. $A_V = -1.5$

$$V^+ = V^- = 0 \text{ (gold)}$$

$$i_s + i_f = 0$$

$$\frac{V_i - V^-}{R_1} + \left(\frac{V^{B+} - V^-}{R_2} + \frac{V_o - V^-}{R_3} \right) = 0 \quad \text{--- 1}$$

$$V^{B+} = V^{B-}$$

$$\Rightarrow \frac{V^{B-} - 0}{R_4} + \frac{V^{B-} - V_o}{R_5} = 0$$

$$\frac{V^{B-}}{R_4} + \frac{V^{B-}}{R_5} - \frac{V_o}{R_5} = 0$$

$$V^{B-} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_o}{R_5}$$

$$V^{B-} = V_o \left(\frac{1}{R_5} \right) \div \left(\frac{R_5 + R_4}{R_4 R_5} \right)$$

$$= V_o \left(\frac{R_4}{R_4 + R_5} \right) \quad \text{--- 2}$$

$$\frac{V_i}{R_1} + \left(\frac{V_o \left(\frac{R_4}{R_4 + R_5} \right)}{R_2} + \frac{V_o}{R_3} \right) = 0$$

$$V_o \left(\frac{\frac{R_4}{R_4 + R_5}}{R_2} + \frac{1}{R_3} \right) = -\frac{V_i}{R_1}$$

$$\therefore A_V = \frac{V_o}{V_i} = -\left(\frac{1}{R_1} \right) \div \left(\frac{\frac{R_4}{R_4 + R_5}}{R_2} + \frac{1}{R_3} \right)$$

$$= -\left(\frac{1}{100} \right) \div \left(\frac{\frac{200}{200+100}}{100} + \frac{1}{100} \right)$$

$$= -0.6$$

$$I_s = I_A + I_B$$

$$I_c = \frac{V_{out} - V_o}{R_5} = \frac{V_o}{R_4}$$

$$\frac{V_i}{R_1} = \frac{0 - V_o}{R_2} + \frac{0 - V_{out}}{R_3}$$

$$\frac{V_{out}}{R_5} - \frac{V_o}{R_5} = \frac{V_o}{R_4}$$

$$\frac{V_i}{R_1} = -\frac{V_o}{R_2} - \frac{V_{out}}{R_3}$$

$$\frac{V_{out}}{R_5} = V_o \left(\frac{1}{R_4} + \frac{1}{R_5} \right)$$

$$\frac{V_i}{R_1} = -\frac{V_{out} \left(\frac{R_4}{R_5 + R_4} \right)}{R_2} - \frac{V_{out}}{R_3}$$

$$V_o = \frac{V_{out}}{R_5} \left(\frac{1}{R_4} + \frac{1}{R_5} \right)^{-1}$$

$$\frac{V_i}{R_1} = -\frac{V_{out} R_4}{R_2 (R_5 + R_4)} - \frac{V_{out}}{R_3}$$

$$= \frac{V_{out}}{R_5} \left(\frac{R_5 R_4}{R_5 + R_4} \right)$$

$$= V_{out} \left(\frac{R_4}{R_5 + R_4} \right)$$

$$\frac{V_i}{R_1} = V_{out} \left(-\frac{R_4}{R_2 (R_5 + R_4)} - \frac{1}{R_3} \right)$$


$$\frac{V_{out}}{V_i} = \frac{1}{R_1} \left(-\frac{R_4}{R_2 (R_5 + R_4)} - \frac{1}{R_3} \right)^{-1}$$

$$= \frac{1}{100} \left(-\frac{200}{100(200+100)} - \frac{1}{100} \right)^{-1}$$

$$= -0.6$$

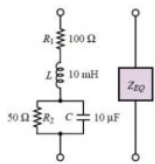Question 5

Which of the following impedances best approximates the equivalent impedance of the following circuit, at frequency $\omega = 10^4$ rad/sec?



- ☐ a. $Z_{EQ} = 100 e^{j\pi/2} \Omega$
- ☐ b. $Z_{EQ} = 100 + 100 e^{j\pi} \Omega$
- ☐ c. $Z_{EQ} = j100 \Omega$
- ☐ d. $Z_{EQ} = 100 + j90 \Omega$

$$\left(\frac{1}{R_2} + j\omega C\right)^{-1}$$

$$= \left(\frac{1 + R_2 j\omega C}{R_2}\right)^{-1}$$

$$= \frac{R_2}{1 + R_2 j\omega C} = \frac{50}{1 + 50j(10^4)(10 \times 10^{-6})}$$

$$= \frac{50}{1 + 5j} \times \frac{1 - 5j}{1 - 5j}$$

$$= \frac{50 - 250j}{26}$$

$$R_2 || C + L + R_1$$

$$\frac{R_2}{1 + R_2 j\omega C} + j\omega L + R_1$$

$$\frac{50}{26} - \frac{250j}{26} + j(10^4)(10 \times 10^{-6}) + 100$$

$$= 101.9 + j90.3$$

Question 3

Evaluate $(5 + 4j)^{-1} (5 - 4j)$ where j is the unitary imaginary number.

- ☐ a. 41
- ☐ b. 9
- ☐ c. $25 + 16j$
- ☐ d. $25 - 16j$

$$\frac{1}{5j} \times \frac{1 - 5j}{1 - 5j}$$

$$= \frac{1 - 5j}{-25}$$

$$= \frac{5j - 1}{25}$$

$$1 \quad 5j$$

$$\begin{array}{|c|c|} \hline 1 & 5j \\ \hline -5j & 25 \\ \hline \end{array}$$

$$-25j^2$$

$$= 25$$

With reference to the figure, determine the equivalent capacitance when $C_1 = 8 \text{ mF}$, $C_2 = 12 \text{ mF}$, $C_3 = 7 \text{ mF}$, $C_4 = 23 \text{ mF}$.

- ☐ a. $C_{eq} = 42 \text{ mF}$
- ☐ b. $C_{eq} = 12 \text{ mF}$
- ☐ c. $C_{eq} = 27 \text{ mF}$
- ☐ d. $C_{eq} = 184 \text{ mF}$

$$\left(\frac{1}{5}\right)^2$$

$$= -1$$

If $V_{in} = 5 \angle 20^\circ$ and $V_{out} = 10 \angle 45^\circ$, in phasor format (amplitude $\angle$ angle), which of the following phasors best represent the ratio V_{out} / V_{in} ?


- ☐ a. $0.5 \angle -15^\circ$
- ☐ b. $15 \angle 65^\circ$
- ☐ c. $2 \angle 15^\circ$
- ☐ d. $5 \angle -15^\circ$

Question 3

Denoting by j the unit imaginary number, which of the following identities is true?

- ☐ a. $|1 + j^2| = \sqrt{2}$
- ☐ b. $j^3 = j$
- ☐ c. $j + \pi = 0$
- ☐ d. $1 + e^{j\pi} = 0$

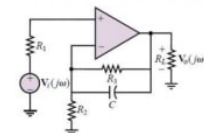The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_c) and pass-band gain (A_v) of the filter.



Given $R_1 = 1 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $R_3 = 10 \text{ k}\Omega$, $C = 100 \text{ nF}$.


- ☐ a. $\omega_c = 2000 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$
- ☐ b. $\omega_c = 250 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$
- ☐ c. $\omega_c = 250 \text{ rad/sec}$; $A_v = 19.08 \text{ dB}$
- ☐ d. $\omega_c = 2000 \text{ rad/sec}$; $A_v = 19.08 \text{ dB}$

$$H = \frac{V_o}{V_i}$$


$$= 1 + \frac{R_3 || C}{R_2}$$

$$= 1 +$$

Capacitors in series/parallel.

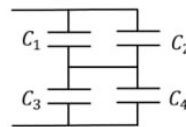


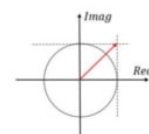The figure below represents the complex plane, a vector (arrow) and the unitary circle.



Which of the following complex numbers best represents the vector?

- ☒ a. $\sqrt{2} e^{j\pi/4}$
- ☐ b. $\sqrt{2}$
- ☐ c. $2 e^{j\pi/2}$
- ☐ d. $2 e^{j\pi}$

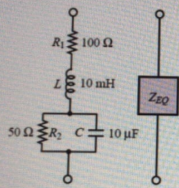Which of the following impedances best approximates the equivalent impedance of the following circuit, at frequency $\omega = 10^4$ rad/sec?

- ☐ a. $Z_{EQ} = j100 \Omega$
☒ b. $Z_{EQ} = 100 + j90 \Omega$ ✓
☐ c. $Z_{EQ} = 100 e^{j\pi/2} \Omega$
☐ d. $Z_{EQ} = 100 + 100 e^{j\pi} \Omega$

$$\left(\frac{1}{R_2} + \frac{1}{j\omega C} \right)^{-1} = \left(\frac{1}{R_2} + j\omega C \right)^{-1}$$

$$= \left(\frac{1 + j\omega C R_2}{R_2} \right)^{-1}$$

$$= \frac{R_2}{1 + j\omega C R_2}$$

$$\therefore Z_{eq} = 100 + j(10^4)(10 \times 10^{-3}) + \frac{50}{1 + j(10^4)(10 \times 10^{-6}) \times 50}$$


$$= 100 + j100 + \frac{50}{1 + j5} \times \frac{1 - j5}{1 - j5}$$

$$= 100 + j100 + \frac{50 - j250}{1 + 25}$$

$$= 100 + j100 + \frac{50}{26} - j\frac{250}{26}$$

$$= \underline{101.923 + j90.384}$$

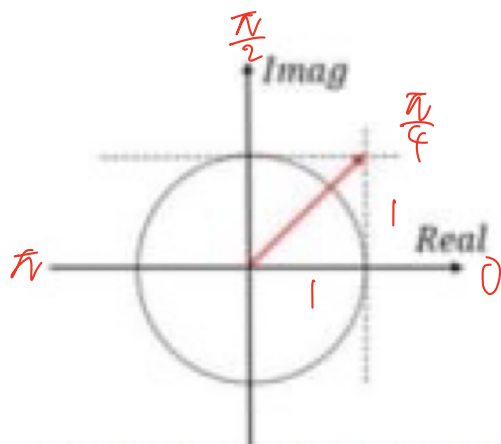The figure below represents the complex plane, a vector (arrow) and the unitary circle.



Which of the following complex numbers best represents the vector?

☒ $\sqrt{2} e^{i\pi/4}$





☐ $\sqrt{2}$

☐ $2 e^{i\pi/2}$

☐ $2 e^{i\pi}$


$$\sqrt{1^2 + 1^2}$$

Capacitors in series/parallel.

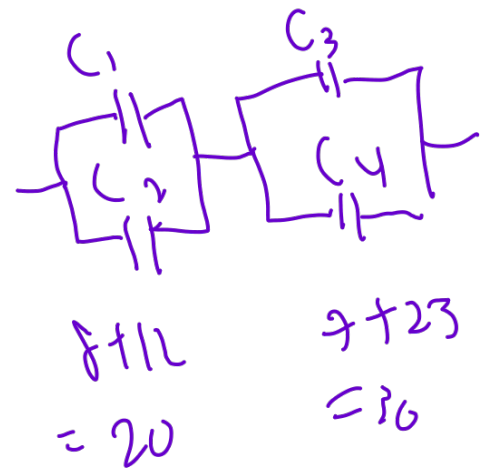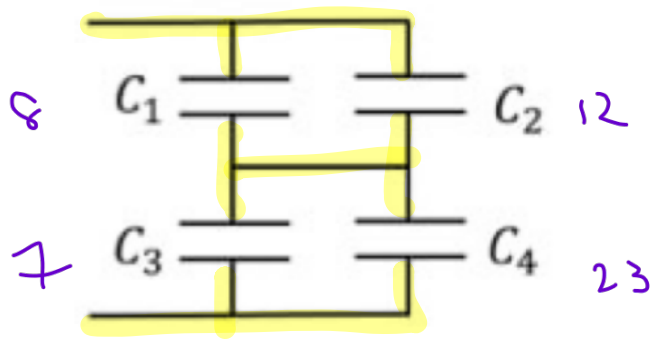

With reference to the figure, determine the equivalent capacitance when $C_1 = 8 \text{ mF}$, $C_2 = 12 \text{ mF}$, $C_3 = 7 \text{ mF}$, $C_4 = 23 \text{ mF}$.

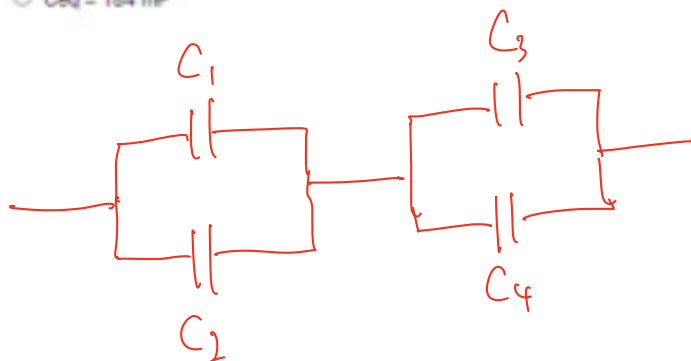- ☐ $C_{eq} = 42 \text{ mF}$
- ☒ $C_{eq} = 12 \text{ mF}$
- ☐ $C_{eq} = 27 \text{ mF}$
- ☐ $C_{eq} = 184 \text{ mF}$



$$C_{eq} = \left(\frac{1}{C_1 + C_2} + \frac{1}{C_3 + C_4} \right)^{-1}$$

$$= \left(\frac{1}{8 + 12} + \frac{1}{7 + 23} \right)^{-1}$$

$$= 12 \text{ mF} //$$

$$\frac{1}{13 + 7} + \frac{1}{11 + 19}$$

$$= \frac{1}{20} + \frac{1}{30}$$

$$\left(\frac{1}{10} + \frac{1}{30} \right)^{-1}$$

$$= 12$$

$$=$$

Question 3

Evaluate $(5 + 4j) \cdot (5 - 4j)$ where j is the unitary imaginary number.

☒ 41

☐ 9

☐ $25 + 16j$

☐ $25 - 16j$

$$(5 + 4j) \times (5 - 4j)$$

$$= 25 - 20j + 20j - 16(-1)$$

$$= 41$$

$$(5 + 4j) \times (5 - 4j)$$

Question 3

Denoting by j the unit imaginary number, which of the following identities is true?

☐ $|1+j^2|=\sqrt{2}$ $\times$

☐ $j^3=j$ $\times$

☐ $j+\pi=0$ $\times$

☐ $1+e^{j\pi}=0$ $\checkmark$

$$|1+j^2|=\sqrt{2}$$

$$|0|=\sqrt{2} \times$$

$$j^3=j \quad j^2j=-j \times$$

$$|1+j^2|=|1-1|=0 \times$$

$$j+\pi = \sqrt{\pi^2+1^2} \angle \tan^{-1}\left(\frac{1}{\pi}\right)$$

$$= 3.296 \angle 0.308 \times$$

$$1+e^{j\pi}=0 \checkmark$$

$$e^{j\pi}=-1$$

$$1 \angle \pi = -1$$

$$|\cos \pi| + |\sin \pi| = -1$$

$$-1+0=-1 //$$

If $V_{in} = 5\angle 20^\circ$ and $V_{out} = 10\angle 45^\circ$, in phasor format (amplitude $\angle$ angle), which of the following phasors best represent the ratio V_{out} / V_{in} ?

- ☐ $0.5\angle -15^\circ$
- ☐ $15\angle 65^\circ$
- ☒ $2\angle 15^\circ$
- ☐ $5\angle -15^\circ$

Question 3

Denoting by j the unit imaginary number, which of the following identities

$$V_{in} = 5\angle 20^\circ$$
$$V_{out} = 10\angle 45^\circ$$

$$\frac{V_{out}}{V_{in}} = \frac{10\angle 45}{5\angle 20}$$
$$= 2\angle 25$$

$$\frac{V_{out}}{V_{in}} = \frac{10\angle 45^\circ}{5\angle 20^\circ}$$
$$= \frac{10e^{j45^\circ}}{5e^{j20^\circ}}$$
$$= 2e^{j25^\circ}$$
$$= 2\angle 25^\circ$$

$$= 1.813\hat{i} + 0.845\hat{j}$$

pic 3:

$$V^- = V^+$$

$$i_s + i_f = 0$$

$$\frac{V_i - V^-}{R_1} + \frac{V_o - V^-}{R_3} + \frac{V^{Bt} - V^-}{R_2} = 0$$

$$\frac{V_i}{R_1} + \frac{V_o}{R_3} + \frac{V^{Bt}}{R_2} = 0 \quad \text{--- (1)}$$

$$V^{Bt} = V_o \times \frac{R_4}{R_4 + R_5} \quad \text{--- (2)}$$

$$\frac{V^{Bt} - 0}{R_4} + \frac{V^{Bt} - V_o}{R_5} = 0$$

$$\frac{V^{Bt}}{R_4} + \frac{V^{Bt}}{R_5} = \frac{V_o}{R_5}$$

$$V^{Bt} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_o}{R_5}$$

$$\begin{aligned} \frac{V_o}{V^{Bt}} &= R_5 \left(\frac{R_5 + R_4}{R_4 R_5} \right) \\ &= \frac{R_5 + R_4}{R_4} \end{aligned}$$

$$\therefore \frac{V_i}{R_1} + \frac{V_o}{R_3} + V_o \frac{R_4}{R_4 + R_5} \times \frac{1}{R_2} = 0$$

$$V_o \left(\frac{1}{R_3} + \frac{R_4}{R_2(R_4 + R_5)} \right) = - \frac{V_i}{R_1}$$

$$\frac{V_o}{V_i} = - \frac{1}{R_1} \times \frac{1}{\left(\frac{1}{R_3} + \frac{R_4}{R_2(R_4 + R_5)} \right)}$$

$$= -0.8 //$$

$$R_1 = R_2 = R_3 = R_4 = 10 \Omega$$

$$R_5 = 30 \Omega$$

pic 5: $V^+ = V^-$

$$I_{in} = 0 = I_s + I_f \quad \text{---} \star$$

$$\frac{V_i - V^+}{R_i} = 0 \quad \text{---} \textcircled{1}$$

$$I_s = -I_f$$

$$- \left(\frac{\frac{V^- - V_0}{R_3}}{1 + j\omega C R_3} + \frac{V^-}{R_2} \right) = 0$$

$$\therefore \frac{V_0}{\frac{R_3}{1 + j\omega C R_3}} = \frac{V^-}{R_2} + \frac{V^-}{\frac{R_3}{1 + j\omega C R_3}}$$

$$V_0 = V^- \left(\frac{1}{R_2} \times \frac{R_3}{1 + j\omega C R_3} + 1 \right)$$

$$V_i = V^- = V^+$$

$$\frac{V_0}{V_i} = \frac{1}{R_2} \times \frac{R_3}{1 + j\omega C R_3} + 1$$

$$\therefore \text{gain} = \frac{R_3}{R_2} + 1$$

$$= 11$$

$$20 \log 11 = 20.83 \text{ dB}$$

$$\omega C R_3 = 1$$

$$\omega = \frac{1}{C R_3} = 200 \text{ rad/s}$$

$$\left(\frac{1}{R_3} + j\omega C \right)^{-1} = \left(\frac{1 + j\omega C R_3}{R_3} \right)^{-1}$$

$$\frac{V_i - V^+}{R_i} = 0$$

$$\frac{V_i}{R_i} - \frac{V^+}{R_i} = 0$$

$$\therefore V_i = V^+ = V^-$$

pic 7

$$V^+ = V^-$$

$$i_{in} = 0 = i_s + i_f$$

$$\frac{V_i - V^+}{R_1} = 0$$

$$\therefore V_i = V^+ = V^- \quad \text{--- (1)}$$

$$\frac{V^-}{R_2} + \frac{V^- - V_o}{\frac{R_3}{1+j\omega C}} = 0$$

$$\frac{V^-}{R_2} + \frac{V^-}{\frac{R_3}{1+j\omega C R_3}} = \frac{V_o}{\frac{R_3}{1+j\omega C R_3}}$$

$$V_o = V^- + \frac{V^-}{R_2} \times \frac{R_3}{1+j\omega C R_3} \quad \text{--- (2)}$$

$$\frac{V_o}{V_i} = 1 + \frac{R_3/R_2}{1+j\omega C R_3} \quad \star$$

$$\text{gain} = 1 + \frac{R_3}{R_2}$$

$$= 1 + \frac{10000}{5000} = 3$$

$$= 20 \log_{10} 3 = 9.54 \text{ dB}$$

$$\omega C R_3 = 1$$

$$\omega = \frac{1}{10000 \times 10000} = 10000 \text{ rad/s}$$

Pic 10

$$V^+ = V^-$$

$$i_{in} = 0 = i_s + i_g$$

$$\frac{V_i - \cancel{V_A} \rightarrow 0}{R_1} + \frac{V_0 - \cancel{V_A} \rightarrow 0}{R_3} + \frac{V^{B+} - \cancel{V_A} \rightarrow 0}{R_2} = 0 \quad \text{--- (1)}$$

$$V^{B+} = V^{B-}$$

$$\frac{V^{B-}}{R_4} + \frac{V^{B-} - V_0}{R_5} = 0$$

$$V^{B-} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_0}{R_5}$$

$$V^{B-} \left(\frac{R_5 + R_4}{R_4 R_5} \right) = \frac{V_0}{R_5}$$

$$V^{B-} = V_0 \left(\frac{R_4}{R_5 + R_4} \right) \quad \text{--- (2)}$$

$$\frac{V_i}{R_1} + \frac{V_0}{R_3} + \frac{V_0}{R_2} \left(\frac{R_4}{R_5 + R_4} \right) = 0$$

$$V_i \left(\frac{1}{R_1} \right) = V_0 \left(-\frac{1}{R_3} - \frac{R_4/R_2}{R_5 + R_4} \right)$$

$$\frac{V_0}{V_i} = \frac{1}{R_1} \div \left(-\frac{1}{R_3} - \frac{R_4/R_2}{R_5 + R_4} \right)$$

$$= -0.6$$

pic 11

$$V^+ = V^-$$

$$i_{in} = 0 = i_c + i_f$$

$$\frac{V_i - V^-}{R_1} + \frac{V_o - V^-}{R_3} + \frac{V^{B1} - V^-}{R_2} = 0 \quad \text{--- (1)}$$

$$\frac{V^{B-}}{R_4} + \frac{V^{B-} - V_o}{R_5} = 0$$

$$V^{B-} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_o}{R_5}$$

$$V^{B-} = V_o \frac{1}{R_5} \left(\frac{R_4 R_5}{R_4 + R_5} \right)$$
$$= V_o \left(\frac{R_4}{R_4 + R_5} \right) \quad \text{--- (2)}$$

$$\frac{V_i}{R_1} + \frac{V_o}{R_3} + \frac{1}{R_2} V_o \frac{R_4}{R_4 + R_5} = 0$$

$$V_o \left(\frac{1}{R_3} + \frac{R_4/R_2}{R_4 + R_5} \right) = V_i \left(-\frac{1}{R_1} \right)$$

$$\therefore \frac{V_o}{V_i} = -\frac{1}{R_1} \div \left(\frac{1}{R_3} + \frac{R_4/R_2}{R_4 + R_5} \right)$$

$$= -0.8 //$$

pic 14

$$V^+ = V^-$$

$$i_{in} = 0 = i_s + i_f$$

$$\frac{V_i - V^+}{R_1} = 0$$

$$\therefore V_i = V^+ = V^- \quad \text{--- (1)}$$

$$\frac{V^-}{R_2} + \frac{V^- - V_o}{\frac{R_3 j\omega C}{R_3 + \frac{1}{j\omega C}}} = 0$$

$$\frac{V^-}{R_2} + \frac{V^-}{1 + j\omega CR_3} = \frac{V_o}{\frac{R_3}{1 + j\omega CR_3}} \quad \text{--- (2)}$$

$$\therefore V_o = V_i \left(1 + \frac{R_3/R_2}{1 + j\omega CR_3} \right)$$

$$\frac{V_o}{V_i} = \left(1 + \frac{R_3/R_2}{1 + j\omega CR_3} \right)$$

$$\begin{aligned} \text{gain} &= 1 + \frac{R_3}{R_2} = 1 + \frac{50000}{5000} = 11 \\ &= 20 \log_{10} 11 \\ &= 20.83 \text{ dB} \end{aligned}$$

$$\omega CR_3 = 1$$

$$\omega = \frac{1}{(10 \times 10^{-9}) \times 50000} = 200 \text{ rad/s}$$

pic 3 $V^+ = V^- = 0$

$$i_{in} = 0 = i_s + i_f$$

$$\frac{V_i - V^-}{R_1} + \frac{V_o - V^-}{R_3} + \frac{V^{2+} - V^-}{R_2} = 0$$

$$\frac{V_i}{R_1} + \frac{V_o}{R_3} + \frac{V^{2+}}{R_2} = 0 \quad \text{--- ①}$$

$$V^{2+} = V^{2-}$$

$$\frac{V^{2-} - 0}{R_4} + \frac{V^{2-} - V_o}{R_5} = 0$$

$$V^{2-} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_o}{R_5}$$

$$V^{2-} = V_o \times \frac{1}{R_5} \left(\frac{1}{R_4} + \frac{1}{R_5} \right)^{-1}$$

$$= V_o \times \frac{1}{R_5} \left(\frac{R_4 + R_5}{R_4 R_5} \right)^{-1}$$

$$= V_o \left(\frac{R_4}{R_4 + R_5} \right) \quad \text{--- ②}$$

$$\frac{V_i}{R_1} + \frac{V_o}{R_3} + V_o \left(\frac{R_4}{R_4 + R_5} \right) \times \left(\frac{1}{R_2} \right) = 0$$

$$\frac{1}{R_1} + \frac{V_o}{V_i} \times \frac{1}{R_3} + \frac{V_o}{V_i} \times \frac{R_4/R_2}{R_4 + R_5} = 0$$

$$\frac{V_o}{V_i} = -\frac{1}{R_1} \div \left(\frac{1}{R_3} + \frac{R_4/R_2}{R_4 + R_5} \right)$$

$$= -0.8 //$$

Pic 5

$$V^+ = V^-$$

$$i_{in} = 0 = i_s + i_f$$

$$\frac{V_i - V^+}{R_1} = 0$$

$$\therefore V_i = V^+ = V^-$$

$$\frac{V^- - 0}{R_2} + \frac{V^- - V_o}{\frac{R_3 \times j\omega C}{R_3 + j\omega C}} = 0$$

$$\frac{V_i}{R_2} + V_i \left(\frac{j\omega C R_3 + 1}{R_3} \right) = V_o \left(\frac{1 + j\omega C R_3}{R_3} \right)$$

$$\therefore \frac{V_o}{V_i} = \left(\frac{1}{R_2} + \frac{j\omega C R_3 + 1}{R_3} \right) \times \left(\frac{R_3}{1 + j\omega C R_3} \right)$$

$$= \frac{1}{R_2} \times \frac{R_3}{1 + j\omega C R_3} + 1$$

$$= \frac{R_3/R_2}{1 + j\omega C R_3} + 1 \quad \begin{array}{l} \rightarrow \text{when } \omega \rightarrow 0, H \rightarrow \frac{R_3/R_2}{1} + 1 \\ \text{when } \omega \rightarrow \infty, H \rightarrow 0 \end{array}$$

$$\therefore \text{gain} = R_3/R_2 + 1 = \frac{50000}{5000} + 1 = 11$$

$$20 \log_{10} 11 = 20.83 \text{ dB} //$$

$$\omega C R_3 = 1$$


$$\omega = \frac{1}{10 \times 10^{-9} \times 50000} = 200 \text{ rad/s} //$$

$$f = \frac{1}{T}$$

$$T = 0.08 \div 0.25$$

$$\therefore f = 28.125 \text{ Hz}$$
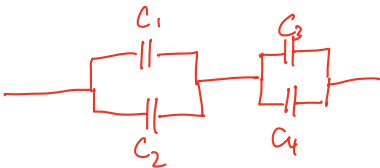
$$\begin{aligned} R_{eq} &= 100 + j\omega L + \frac{50 \frac{j\omega C}{50 + \frac{j\omega C}{50}}}{1 + j\omega C 50} \times \frac{1 - j\omega C 50}{1 - j\omega C 50} \\ &= 100 + j\omega L + \frac{50}{1 + j\omega C 50} \times \frac{1 - j\omega C 50}{1 - j\omega C 50} \\ &= 100 + j\omega L + \frac{50 - j\omega C 250}{1 + \omega^2 C^2 \times 50^2} \\ &= 101.923 + j99.038 \, \Omega \end{aligned}$$



$$\begin{aligned} C_{eq} &= \left(\frac{1}{C_1 + C_2} + \frac{1}{C_3 + C_4} \right)^{-1} \\ &= \left(\frac{1}{20} + \frac{1}{30} \right)^{-1} \\ &= 12 \text{ mF} \end{aligned}$$

$$(5 + j4)(5 - j4)$$

$$= 25 + 16 = 41 //$$

$$\frac{10 \angle 45^\circ}{5 \angle 20^\circ} = 2 \angle 25^\circ$$



$$\begin{aligned} |1 + j^2| &= |1 + (-1)| = 0 \neq \sqrt{2} \\ j^3 &= j^2 j = -1j = -j \neq j \\ \pi + j &= \sqrt{\pi^2 + 1} \angle \tan^{-1} \frac{1}{\pi} \neq 0 \end{aligned} \quad \left. \vphantom{\begin{aligned} |1 + j^2| &= |1 + (-1)| = 0 \neq \sqrt{2} \\ j^3 &= j^2 j = -1j = -j \neq j \\ \pi + j &= \sqrt{\pi^2 + 1} \angle \tan^{-1} \frac{1}{\pi} \neq 0 \end{aligned}} \right\} \times$$

$$\left. \begin{aligned} 1 + e^{j\pi} &= 0 \\ 1 + 1 \angle \pi &= 0 \\ 1 + (-1) &= 0 \end{aligned} \right\} \checkmark$$

CA2

1)

actual

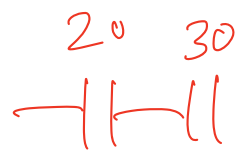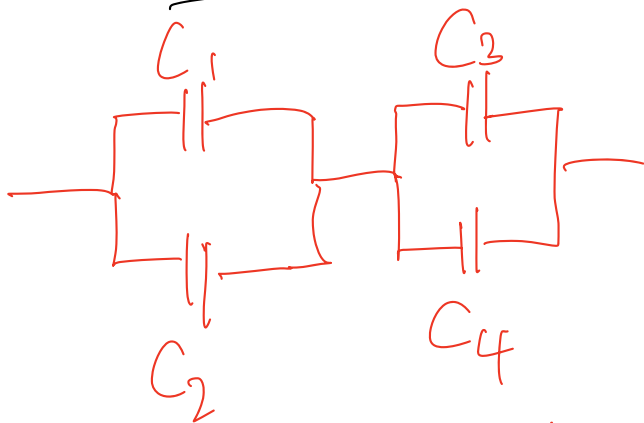

$$C_{eq} = \left(\frac{1}{13+7} + \frac{1}{7+23} \right)^{-1}$$

$$= 12 \text{ mF}$$

$$\begin{aligned} 2) & 100 + j\omega L + \frac{50 \times \frac{1}{j\omega C}}{50 + \frac{1}{j\omega C}} \\ &= 100 + j100 + \frac{50}{50j\omega C + 1} \times \frac{1 - j\omega C 50}{1 - j\omega C 50} \\ &= 100 + j100 + \frac{50 - j2500\omega C}{1 + (\omega C 50)^2} \\ &= 100 + \frac{50}{1 + (50\omega C)^2} + j100 - j \left(\frac{2500\omega C}{1 + (50\omega C)^2} \right) \end{aligned}$$

$$= 101.923 + j 90.38$$

$$= 100 + j 90 \Omega$$

$$3) |1+j^2| = |1+(-1)| = 0 \neq \sqrt{2}$$

$$j^3 = j^2 j = -1j = -j \neq j$$

$$\bar{a} + j \neq 0$$

$$1 + e^{j\pi} = 1 + 1\angle\pi = 1 + \cos\pi + j\sin\pi \\ = 1 + (-1) = 0 \quad \checkmark$$

$$4) R_1 = R_2 = R_3 = R_5 = 10\Omega, R_4 = 20\Omega$$

$$V^+ = V^- = 0$$

$$i_{in} = 0 = i_s + i_f$$

$$\frac{V_i - V^-}{R_1} + \frac{V_o - V^-}{R_3} + \frac{V^{2+} - V^-}{R_2} = 0$$

$$\frac{V_i}{R_1} + \frac{V_o}{R_3} + \frac{V^{2+}}{R_2} = 0 \quad \text{--- (1)}$$

$$V^{2+} = V^{2-}$$

$$\frac{V^{2-} - 0}{R_4} + \frac{V^{2-} - V_o}{R_5} = 0$$

$$V^{2-} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_o}{R_5}$$

$$V^{2-} = V_o \left(\frac{1}{R_5} \right) \left(\frac{1}{R_4} + \frac{1}{R_5} \right)^{-1}$$

$$= V_o \left(\frac{1}{R_5} \right) \left(\frac{R_5 + R_4}{R_4 R_5} \right)^{-1}$$

$$= V_o \left(\frac{R_4}{R_5 + R_4} \right) \quad \text{--- (2)}$$

$$\therefore \frac{V_i}{R_1} + \frac{V_o}{R_3} + V_o \left(\frac{R_4/R_2}{R_5 + R_4} \right) = 0$$

$$\therefore \frac{V_o}{V_i} = -\frac{1}{R_1} \div \left(\frac{1}{R_3} + \frac{R_4/R_2}{R_5 + R_4} \right) \\ = -0.6$$

$$5) R_1 = 2k\Omega, R_2 = 60k\Omega, R_3 = 100k\Omega, C = 100nF$$

$$V^+ = V^- = V_i$$

$$i_{in} = 0 = i_s + i_f$$

$$\frac{V^-}{R_2} + \frac{V^- - V^0}{\frac{R_3 \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}}} = 0$$

$$V_i \left(\frac{1}{R_2} \right) + V_i \left(\frac{R_3 + \frac{1}{j\omega C}}{R_3 \frac{1}{j\omega C}} \right) = V_o \left(\frac{R_3 + \frac{1}{j\omega C}}{R_3 \frac{1}{j\omega C}} \right)$$

$$1 + \left(\frac{1}{R_2} \right) \times \frac{R_3 \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} = \frac{V_o}{V_i}$$

$$\frac{V_o}{V_i} = 1 + \frac{1}{R_2} \left(\frac{R_3}{1 + j\omega C R_3} \right)$$

$$= 1 + \frac{R_3 / R_2}{1 + j\omega C R_3}$$

$$\omega = \frac{1}{C R_3}$$

$$= \frac{1}{100 \times 10^{-9} \times 100000} = 100 \text{ rad/s}$$

$$\text{gain} = 1 + \frac{R_3}{R_2}$$


$$= 1 + \frac{100000}{10000}$$

$$= 11$$

$$20 \log_{10} 11 = 20.83 \text{ dB}$$

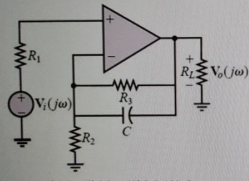Question 3

The circuit shown in the figure is an active filter with. Determine the cutoff frequency (ω_c) and pass-band gain (A_v) of the filter.



Given $R_1 = 2k\Omega$, $R_2 = 5k\Omega$, $R_3 = 20k\Omega$, $C = 100nF$.

- ☐ $\omega_c = 500 \text{ rad/sec}$; $A_v = 13.98 \text{ dB}$.
- ☐ $\omega_c = 500 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$.
- ☐ $\omega_c = 2000 \text{ rad/sec}$; $A_v = 8.22 \text{ dB}$.
- ☐ $\omega_c = 2000 \text{ rad/sec}$; $A_v = 13.98 \text{ dB}$.

$$V^+ = V^-$$

$$I_{in} = 0 = I_S + I_F$$

$$\frac{V_i - V^+}{R_1} = 0$$

$$V_i = V^+ \quad \text{--- (1)}$$

$$\frac{V^- - 0}{R_2} + \frac{V^- - V_o}{\frac{1}{1 + j\omega C R_3}} = 0$$

$$V^- \left(\frac{1}{R_2} + \frac{1 + j\omega C R_3}{R_3} \right) = V_o \left(\frac{1 + j\omega C R_3}{R_3} \right)$$

$$\therefore V_{in} \left(\frac{1}{R_2} + \frac{1 + j\omega C R_3}{R_3} \right) = V_o \left(\frac{1 + j\omega C R_3}{R_3} \right) = \frac{R_3}{1 + j\omega C R_3}$$

$$\frac{V_o}{V_{in}} = \frac{\left(\frac{1}{R_2} + \frac{1 + j\omega C R_3}{R_3} \right)}{\left(\frac{1 + j\omega C R_3}{R_3} \right)}$$

$$= \frac{1}{R_2} \times \frac{R_3}{1 + j\omega C R_3} + 1$$

$$= 1 + \frac{R_3/R_2}{1 + j\omega C R_3}$$

$$\text{gain} = \left| \frac{V_{out}}{V_{in}} \right|$$

$$\omega C R_3 \approx 1$$

$$\omega = \frac{1}{C R_3}$$

$$= \frac{1}{100 \times 10^{-9} \times 20000}$$

$$= 500 \text{ rad/s}$$

$$\text{when } \omega \rightarrow 0, |H| = 1 + \frac{R_3}{R_2}$$

$$\omega \rightarrow \infty, |H| = 1$$

$\therefore$ Low Pass filter

$$\text{gain} = 1 + \frac{R_3}{R_2} = 5$$

$$20 \log_{10} 5 = 13.98 \text{ dB}$$