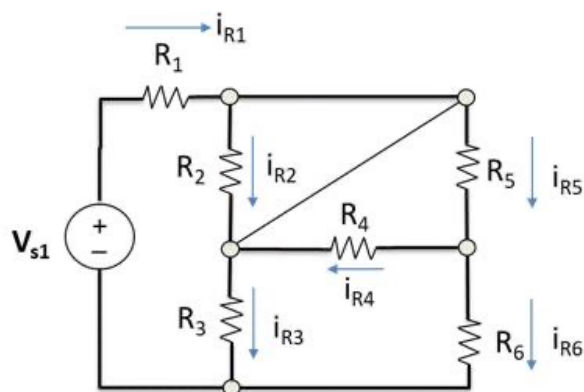


What's the current in R_3 , i.e., i_{R3} , in the following circuit? (Hint: use supernode)




Given $i_{R1} = 7.5\text{A}$, $i_{R5} = 2.5\text{A}$, $i_{R6} = 5.5\text{A}$

Which among the following values most closely matches the correct answer?

- ☐ a. 2.5A
- ☐ b. 3.0A
- ☐ c. 2.0A
- ☐ d. 1.5A

$$i_{R3} = i_{R1}(\text{question}) - i_{R6}(\text{question})$$

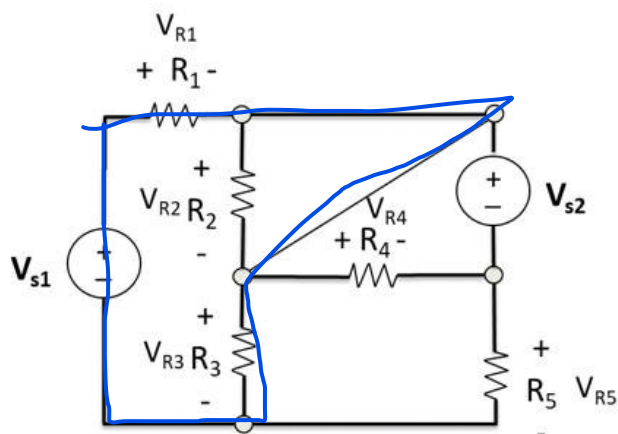What's the voltage across R_3 , i.e., V_{R3} , in the following circuit? (Hint: label different node with different color)




Given $V_{R1} = 8\text{V}$, $V_{R5} = 1\text{V}$, $V_{S1} = 10\text{V}$, and $V_{S2} = 1\text{V}$

Which among the following values most closely matches the correct answer?

- ☐ a. 1V
- ☐ b. 3V
- ☐ c. 4V
- ☐ d. 2V

own notes: $-V_{s1}(\text{question}) + V_{r1}(\text{question}) + V_{r3} = 0$

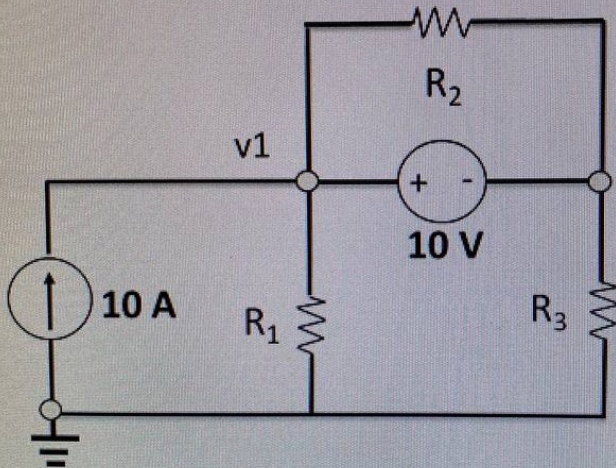In the circuit below, what is the Thevenin (open-circuit) voltage when R_3 is the load?




Given $R_1 = R_2 = R_3 = 8 \, \Omega$

Which among the following values most closely matches the correct answer?

- ☐ a. 65V
- ☐ b. 75V
- ☐ c. 60V
- ☐ d. 70V

own notes: $10A(\text{given}) \times R(\text{question}) - 10V(\text{given}) =$

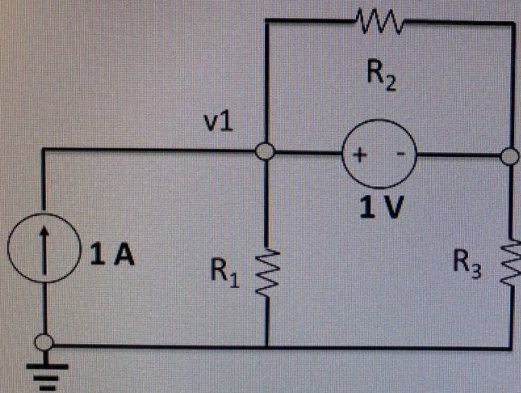In the circuit below, what is the Norton (short-circuit) current when R_3 is the load?



Given $R_1 = 2.5 \, \Omega$, $R_2 = 1 \, \Omega$ Which among the following values most closely matches the correct answer?

- ☐ a. 0.8A
- ☐ b. 0.5A
- ☐ c. 0.6A
- ☐ d. 0.7A


$$i_b(R_2) - (i_a - i_b)(R_1) = 0$$

[this is the formula I used, but I got it wrong
not sure if it my careless mistake or the formula wrong]

find i_b , with i_a given in the diagram, and R_1 and R_2 in the question

What's the equivalent resistance seen by V_{s1} in the following circuit?
with different color)

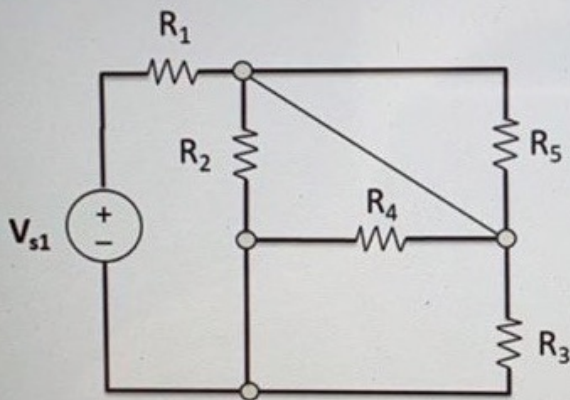(Hint: label different node with different color)



Given $R_1 = 1 \Omega$, $R_2 = 1 \Omega$, $R_3 = 1 \Omega$, $R_4 = 1 \Omega$, $R_5 = 2 \Omega$

Which among the following values most closely matches the correct answer?

- ☐ a. 1.3Ω
- ☐ b. 2.6Ω
- ☐ c. 3.6Ω
- ☐ d. 1.6Ω

$$R_T = (R_3 \parallel R_4 + R_5) \parallel R_2 + R_1$$


$$= 1.714 \Omega$$

Question 1



In the circuit below, what is the node voltage v_1 ?

Given $R_1 = R_2 = R_3 = 110\ \Omega$

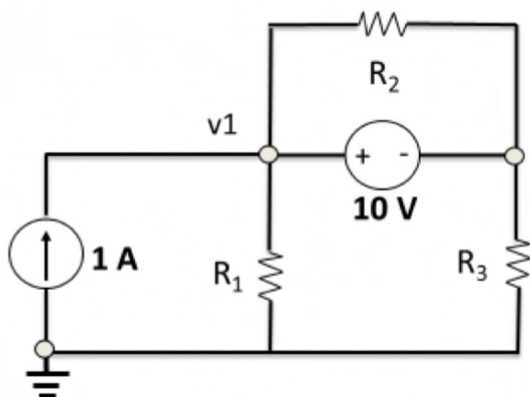

Selected Answer: ☒ 60.0 V

Answers: 65.0 V

30.0 V

35.0 V

☒ 60.0 V

$$R_2 i_1 + 10 = 0 \rightarrow i_1 = \frac{1}{11}$$

$$-10 + R_3 i_2 + R_1 (i_2 - 1) = 0$$

$$-10 + i_2 (R_3 + R_1) - R_1 = 0 \rightarrow i_2 = \frac{6}{11}$$

since node on R_3 = node on R_1 ,

$$i_2 R_3 = V_1$$

$$V_1 = \frac{6}{11} (110)$$

$$= 60$$


Question 2

20 of



What's the equivalent resistance seen by R_4 in the following circuit? (Hint: short circuit V_{s1} and V_{s2})

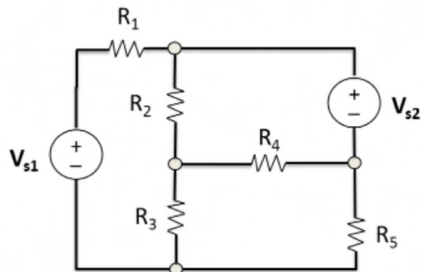Given $R_1 = R_2 = R_3 = R_4 = R_5 = 13\ \Omega$



Selected Answer: ☒ 7.8 Ω

Answers: ☐ 6.8 Ω

☒ 7.8 Ω

☐ 9.8 Ω

☐ 8.8 Ω


$$R_4 = [(R_1 \parallel R_5) + R_2] \parallel R_3$$

$$= 7.8\ \Omega$$

Question 3



Referring to the following circuit

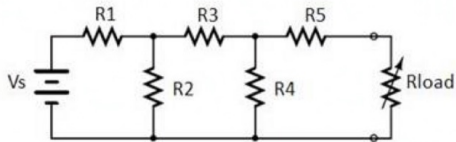

and knowing that

$V_s = 10 \text{ [V]}$
 $R_1 = 10.1 \text{ [Ohms]}$
 $R_2 = 9.5 \text{ [Ohms]}$
 $R_3 = 2.3 \text{ [Ohms]}$
 $R_4 = 3.3 \text{ [Ohms]}$
 $R_5 = 5.5 \text{ [Ohms]}$

determine the value of R_{load} which ensures maximum power transfer.

Allowing for some numerical approximation, which among the following values most closely matches the correct answer?

Selected Answer: ☒ $R_{load} = 7.7624 \text{ [Ohms]}$

Answers: $R_{load} = 15.5248 \text{ [Ohms]}$

$R_{load} = -2.2376 \text{ [Ohms]}$

☒ $R_{load} = 7.7624 \text{ [Ohms]}$


$R_{load} = 30.7 \text{ [Ohms]}$

$$R_1 = [(R_1 || R_2) + R_3] || R_4 + R_5$$
$$= 7.7624 \Omega$$

Question 4



Referring to the following circuit

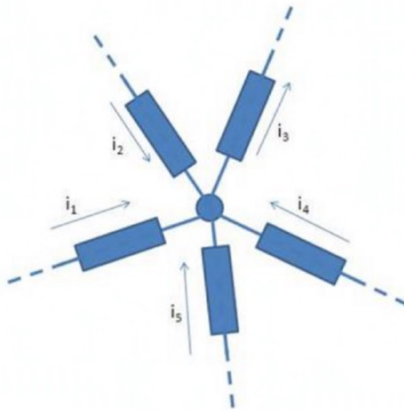

and knowing that

$i_1 = 9.1 \text{ [A]}$
 $i_2 = -2.4 \text{ [A]}$
 $i_3 = -1.9 \text{ [A]}$
 $i_4 = -11.9 \text{ [A]}$

determine the value of i_5 .

Allowing for some numerical approximation, which among the following values most closely matches the correct answer?

Selected Answer: ☒ $i_5 = 3.3 \text{ A}$

Answers: ☐ $i_5 = -3.3 \text{ A}$

☐ $i_5 = -1.3 \text{ A}$

☐ $i_5 = 0.3 \text{ A}$


☒ $i_5 = 3.3 \text{ A}$

$$\begin{aligned} i_1 + i_2 + i_4 + i_5 &= i_3 \\ i_5 &= i_3 - i_1 - i_2 - i_4 \\ &= 3.3 \text{ A} \end{aligned}$$

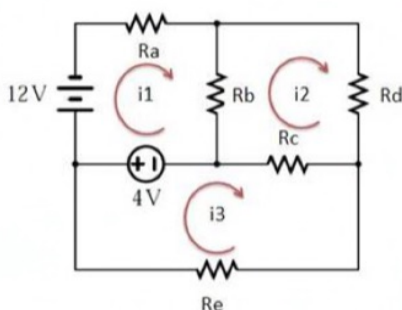Question 5



The mesh-current method, applied to the following circuit



will lead to a 3x3 system of equations such as

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -8V \\ 0V \\ -4V \end{bmatrix}$$

Allowing for some numerical approximation and knowing

$R_a = 3.1$ [Ohms]
 $R_b = 4.5$ [Ohms]
 $R_c = 20.2$ [Ohms]
 $R_d = 20.3$ [Ohms]
 $R_e = 15.5$ [Ohms]

which among the following matrices best represents the resistance matrix $[R_{ij}]$ in the equation above?

Selected Answer:

$$\begin{bmatrix} 7.6 & -4.5 & 0 \\ -4.5 & 45 & -20.2 \\ 0 & -20.2 & 35.7 \end{bmatrix}$$

$$12V + i_1 R_a + (i_1 - i_2) R_b - 4V = 0$$

$$i_1 (R_a + R_b) - R_b i_2 = -8V$$

Answers:

$$\begin{bmatrix} 7.6 & 0 & 0 \\ 0 & 45 & 0 \\ 0 & 0 & 35.7 \end{bmatrix}$$

$$(i_2 - i_1) R_b + i_2 R_d + (i_2 - i_3) R_c = 0$$

$$-R_b i_1 + i_2 (R_b + R_d + R_c) - R_c i_3 = 0$$

$$\begin{bmatrix} 7.6 & -4.5 & -20.2 \\ 0 & 45 & 40.6 \\ 0 & 0 & 35.7 \end{bmatrix}$$

$$4V + (i_3 - i_2) R_c + i_3 R_e = 0$$

$$-R_c i_2 + i_3 (R_c + R_e) = -4V$$

$$\begin{bmatrix} 3.1 & 4.5 & 20.2 \\ 4.5 & 20.3 & 15.5 \\ 20.2 & 15.5 & 18.6 \end{bmatrix}$$

$$\begin{bmatrix} 7.6 & -4.5 & 0 \\ -4.5 & 45 & -20.2 \\ 0 & -20.2 & 35.7 \end{bmatrix}$$