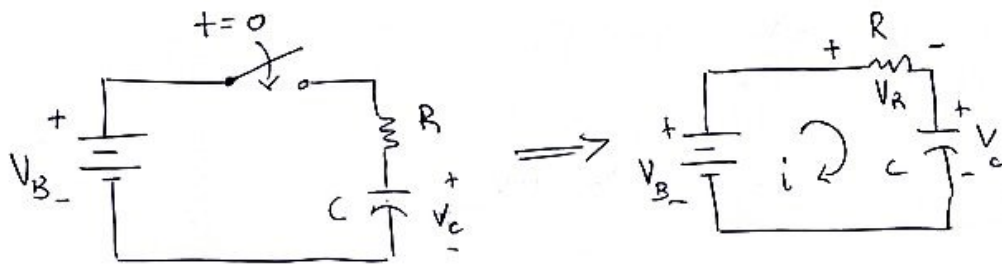


1. (i)



KVL (at $t \geq 0$)

$$V_B = V_R + V_C \quad (1)$$

$$V_R = i \cdot R \quad (2)$$

$$i = C \frac{d}{dt} V_C \quad (3)$$

Sub. (3) in (2),

$$V_R = C \frac{d}{dt} V_C \cdot R \quad (4)$$

Sub. (4) in (1),

$$V_B = C \frac{d}{dt} V_C \cdot R + V_C$$

$$\frac{d}{dt} V_C = -\frac{1}{RC} V_C + \frac{V_B}{RC} \quad (5) \quad \frac{V}{t} = \frac{V}{\text{sec}}$$

Initial condition,

$$V_C (t=0) = 0V$$

Final condition,

$$V_C (t=\infty) = V_\infty = ?$$

$$\frac{dV_{\infty}}{dt} = -\frac{1}{RC} V_{\infty} + \frac{V_B}{RC}$$

$$-\frac{1}{RC} \cdot V_{\infty} + \frac{V_B}{RC} \quad \text{--- (6)}$$




$$V_c(t=\infty) \Rightarrow V_{\infty} = V_B = \underline{\underline{6V}}$$

(ii) $Z = RC = 1K\Omega \cdot 1mF = 1s$

(iii)+(iv) $V_c(t)$ for $t > 0$

$$V_c(t) = (V_0 - V_{\infty}) \cdot e^{-\frac{t}{Z}} + V_{\infty}$$

$V_0 = 0V$
 $V_{\infty} = 6V$
 $Z = 1s.$

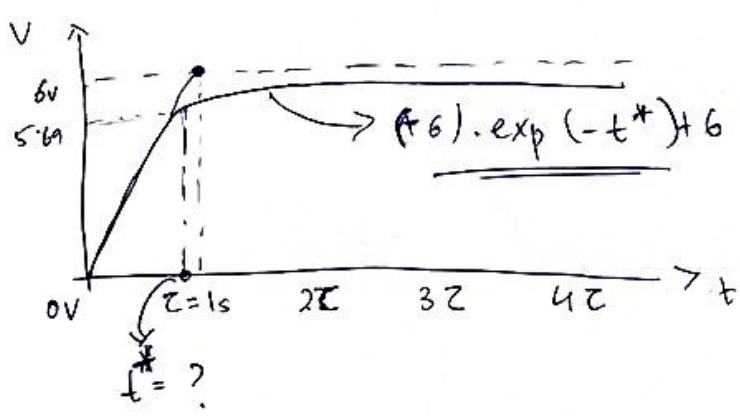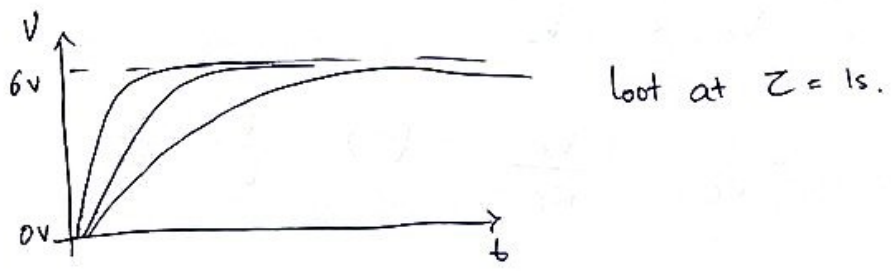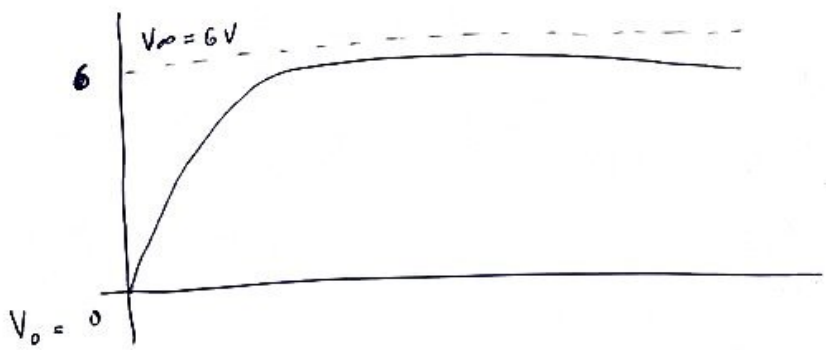

$$(v) \quad E = \frac{1}{2} CV^2$$

$$(vi) \quad E_{\max} = \frac{1}{2} CV_{\max}^2 = \frac{1}{2} \cdot 1\text{mF} \cdot (6V)^2 = 18\text{mJ}$$


$$E_{90\%} = 90\% E_{\max} = \frac{1}{2} C (V_{90\%})^2$$

$$V_{90\%} = \sqrt{\frac{2 \cdot 16 \cdot 2}{1\text{mF}}} = 5.69V$$

$$V_{90\%} = 5.69 = -6 \cdot \exp(-t^*) + 6$$

$$t^* = -\ln\left(\frac{6 - V_{90\%}}{6}\right) = 2.96s$$

2.(i)

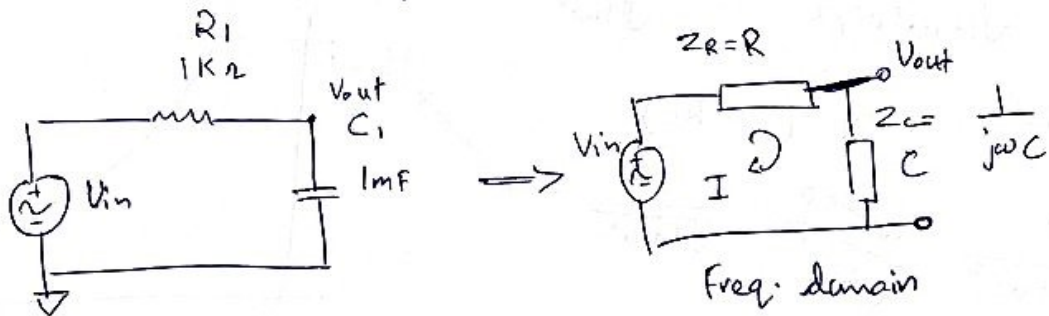

$$I = \frac{V_{in}}{Z_R + Z_C} = \frac{V_{in}}{R + \frac{1}{j\omega C}} \quad (1)$$

$$V_{out} = I \cdot Z_C = I \cdot \frac{1}{j\omega C} \quad (2)$$

Sub. (1) in (2),

$$V_{out} = \frac{V_{in}}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C} = \frac{V_{in}}{1 + j\omega RC} \quad (3)$$

$\tau = RC = 1s$

$$(ii) \quad H = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega}$$

$\tau = 1s$

(iii) $|H| \rightarrow$ Amplitude
 $\angle H \rightarrow$ Phase

$$z = a + jb$$

$$|z| = \sqrt{a^2 + b^2} \rightarrow \text{Amp.}$$

$$\frac{1}{z} = \frac{1}{\sqrt{a^2 + b^2}}$$


$$\angle z = \tan^{-1}\left(\frac{b}{a}\right) \rightarrow \text{Phase}$$

$$\angle \frac{1}{z} = -\tan^{-1}\left(\frac{b}{a}\right)$$

$$|H| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{1 + \omega^2}}$$

$$\angle H = -\tan^{-1}(\omega RC)$$
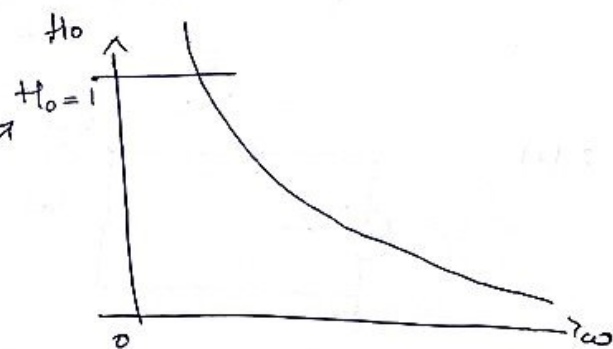
$$\frac{1}{\sqrt{1 + \omega^2}} \begin{matrix} \xrightarrow{\omega \rightarrow 0} \\ \xrightarrow{\omega \rightarrow \infty} \end{matrix} \begin{matrix} \frac{1}{\sqrt{1 + 0^2}} = 1 \\ \frac{1}{\sqrt{1 + \omega^2}} \propto \frac{1}{\omega} \end{matrix}$$



$$|H(j\omega_0)| = \frac{H_0}{\sqrt{2}}$$

$$\frac{1}{\sqrt{1 + \omega_0^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\sqrt{1 + \omega_0^2 R^2 C^2} = \sqrt{2}$$

$$1 + \omega_0^2 R^2 C^2 = 2$$

$$\omega_0^2 R^2 C^2 = 1$$

$$\omega_0 = \frac{1}{RC} = 1 \text{ rad/s}$$

(iv) $\omega_0 = 2\pi f_0$

$$f_0 = \frac{1}{2\pi} = 0.159 \text{ Hz}$$