



NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE

MA3005 Control Theory

Tutorial 10

Mir Feroskhan

Question 1

Consider the following model of a spacecraft (same as in Tutorial 9) with a Proportional-Velocity (PV) controller

1. Find the gains K_p and K_v that yield a pair of dominant closed-loop poles at $s = -1 \pm j$.
2. Compare the step responses of the PV controller and of the PD controller designed in Tutorial 9.

1.

$$\text{CLTF: } \frac{C(s)}{R(s)} = \frac{\frac{K_p}{s^2 + K_p K_v s}}{1 + \frac{K_p}{s^2 + K_p K_v s}} = \frac{K_p}{s^2 + K_p K_v s + K_p}$$

CE: $s^2 + K_p K_v s + K_p = 0$

Subst

$s = -1 + j$: $(-1 + j)^2 + K_p K_v (-1 + j) + K_p = 0$

$$-2j - K_p K_v + K_p K_v j + K_p = 0$$


$$-K_p K_v + K_p + (K_p K_v - 2)j = 0$$


$$\Rightarrow -K_p K_v + K_p = 0 \quad \Rightarrow K_p K_v - 2 = 0$$


$$K_p = 2 \quad \leftarrow K_p K_v = 2$$

$$K_v = 1$$
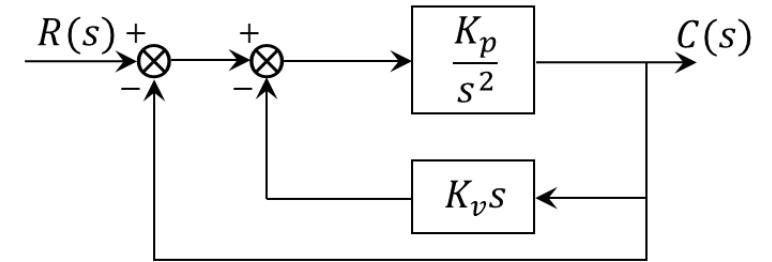
$$\frac{C(s)}{R(s)} = \frac{2}{s^2 + 2s + 2}$$


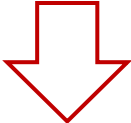
$$TF = \frac{\frac{K_p}{s^2}}{1 + \frac{K_p}{s^2} K_v s} = \frac{\frac{K_p}{s^2}}{\frac{s^2 + K_p K_v s}{s^2}} = \frac{K_p}{s^2 + K_p K_v s}$$

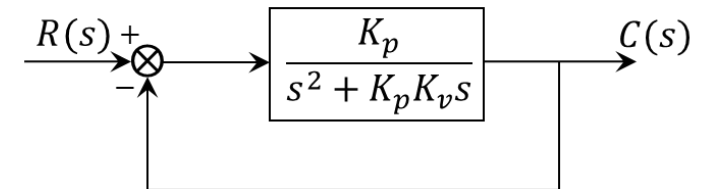


Question 1

Consider the following model of a spacecraft (same as in Tutorial 9) with a Proportional-Velocity (PV) controller


1. Find the gains K_p and K_v that yield a pair of dominant closed-loop poles at $s = -1 \pm j$.
2. Compare the step responses of the PV controller and of the PD controller designed in Tutorial 9.

2. With PV Controller, $K_v s = s$:
$$\frac{C(s)}{R(s)} = \frac{2}{s^2 + 2s + 2}$$

With PD Controller, $G_c(s) = K(s + z_c) = 2(s + 1)$:

$$\frac{C(s)}{R(s)} = \frac{2(s + 1)}{s^2 + 2s + 2}$$

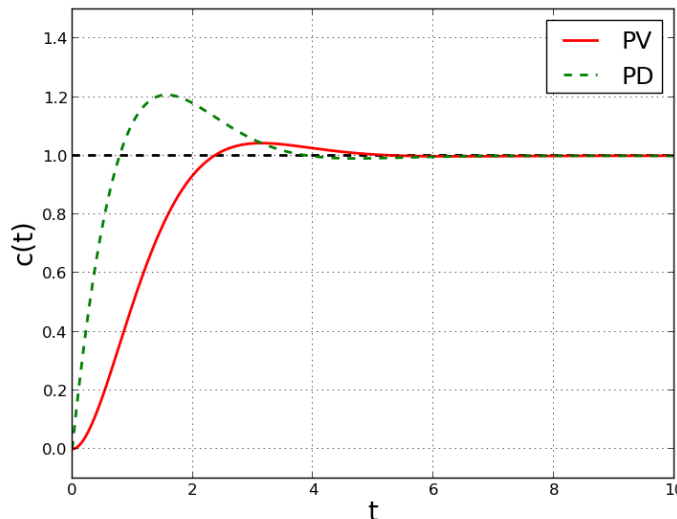There's an "s" term in the numerator $\Rightarrow$ Not a "pure" 2nd order system




With PV Controller

Rise Time: 1.52
Settling Time: 4.22
Overshoot: 4.32
Peak: 1.04
Peak Time: 3.13

With PD Controller

Rise Time: 0.60
Settling Time: 3.46
Overshoot: 20.79
Peak: 1.21
Peak Time: 1.57

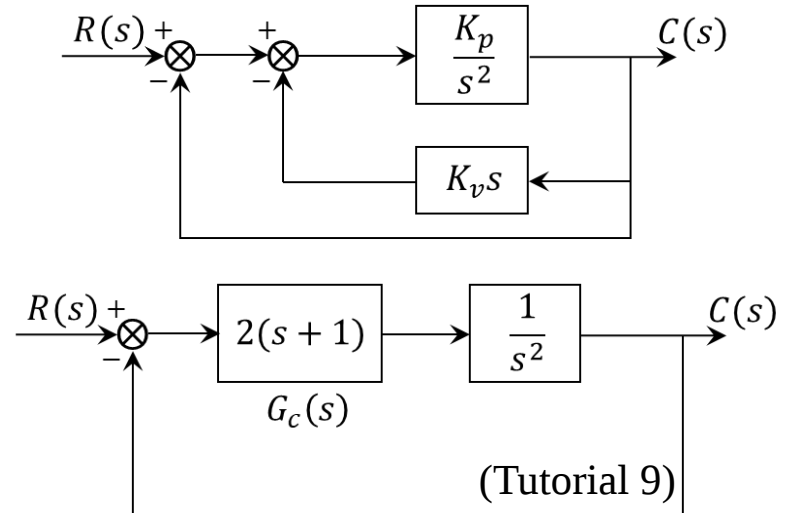$\Rightarrow$ Different transient response with similar settling time
 $\Rightarrow$ PD may increase overshoot




MATLAB script:

```
PV1=2;PV2=[1 2 2];
PD1=[2 2];PD2=[1 2 2];
PV_sys=tf(PV1,PV2);
PD_sys=tf(PD1,PD2);

time=0:0.1:10;
PV=step(PV_sys,time);
PD=step(PD_sys,time);
PV_info = stepinfo(PV_sys);
PD_info = stepinfo(PD_sys);

figure
plot(time,PV,time,PD);
```

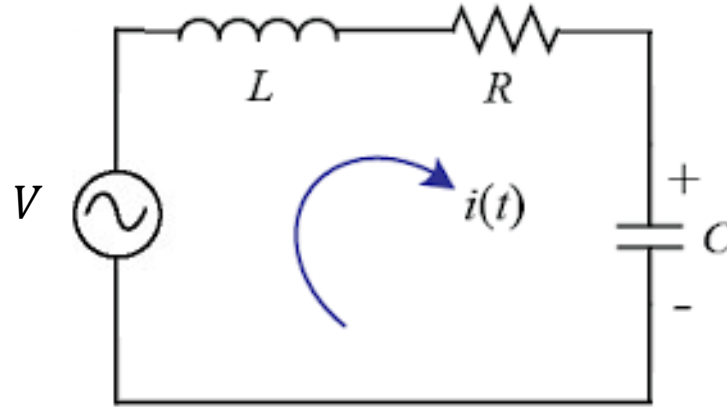Background on Electrical and Electronic Systems



$$V_L(t) + V_R(t) + V_C(t) = V(t)$$

$$L \frac{di(t)}{dt} + R i(t) + \frac{1}{C} \int i dt = V(t)$$

For resistor:

$$V_R(t) = R i(t)$$

$$V_R(s) = R I(s)$$

$$V_R(j\omega) = R I(j\omega)$$

For capacitor:

$$V_C(t) = \frac{1}{C} \int i dt$$

$$\frac{dV_C(t)}{dt} = \frac{1}{C} i(t)$$

$$V_C(s) = \frac{1}{Cs} I(s)$$

$$V_C(j\omega) = \frac{1}{j\omega C} I(j\omega)$$

“resistance” of capacitor

For inductor:

$$V_L(t) = L \frac{di(t)}{dt}$$

$$V_L(s) = Ls I(s)$$

$$V_L(j\omega) = j\omega L I(j\omega)$$

“resistance” of inductor

Impedance is the frequency domain ratio of the voltage to the current

$$Z_R(j\omega) = R$$

$$Z_L(j\omega) = j\omega L$$

$$Z_C(j\omega) = \frac{1}{j\omega C}$$

Question 2

Consider the following circuit:


1. Show that the circuit has the following transfer function

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \frac{j \frac{\omega}{\omega_1}}{(1 + j \frac{\omega}{\omega_1})(1 + j \frac{\omega}{\omega_2})} \quad \text{where } \omega_1 = \frac{1}{R_1 C_1} \text{ and } \omega_2 = \frac{1}{R_2 C_2}$$

$$\begin{aligned} Z_1 &= R_1 + \frac{1}{j\omega C_1} \\ &= R_1 + \frac{R_1}{j\omega R_1 C_1} \\ &= \frac{R_1 j\omega R_1 C_1}{j\omega R_1 C_1} + \frac{R_1}{j\omega R_1 C_1} \\ &= \frac{R_1}{j\omega R_1 C_1} (j\omega R_1 C_1 + 1) \\ &= \frac{R_1 (1 + j \frac{\omega}{\omega_1})}{j \frac{\omega}{\omega_1}} \end{aligned}$$

$$\begin{aligned} Z_2 &= R_2 \parallel \frac{1}{j\omega C_2} \\ \frac{1}{Z_2} &= \frac{1}{R_2} + \frac{j\omega C_2}{1} \\ \Rightarrow Z_2 &= \frac{R_2}{1 + j\omega C_2 R_2} \\ &= \frac{R_2}{1 + j \frac{\omega}{\omega_2}} \end{aligned}$$
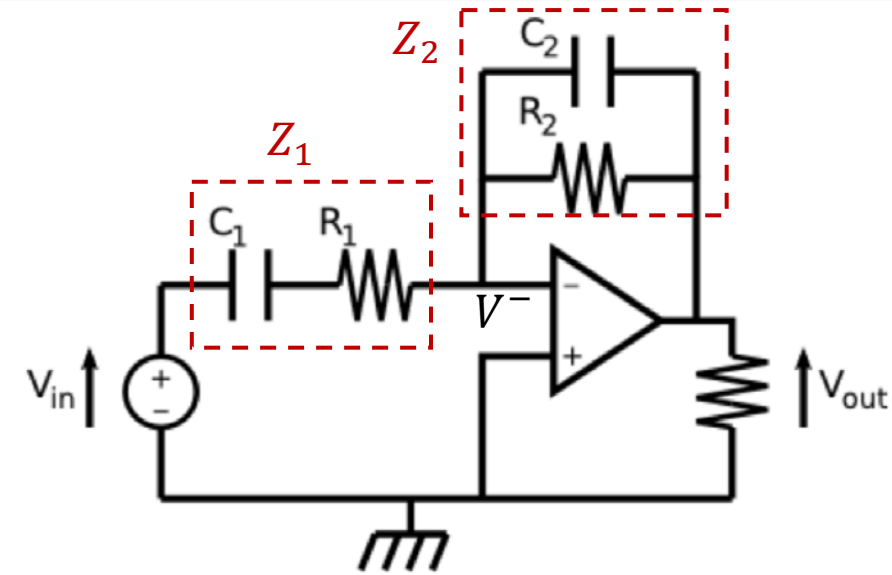
$$\begin{aligned} Z_R(j\omega) &= R \\ Z_L(j\omega) &= j\omega L \\ Z_C(j\omega) &= \frac{1}{j\omega C} \end{aligned}$$



Note: In ideal op amp, no current flows into the input terminals

$$i^- = 0 \rightarrow \frac{V_{in} - V^-}{Z_1} = \frac{V^- - V_{out}}{Z_2}$$

$$V^- = 0 \rightarrow \frac{V_{in}}{Z_1} = \frac{-V_{out}}{Z_2}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-Z_2}{Z_1} = \frac{-R_2}{R_1} \frac{(j \frac{\omega}{\omega_1})}{(1 + j \frac{\omega}{\omega_1})(1 + j \frac{\omega}{\omega_2})}$$

Question 2

2. From now on, assume the following numerical values: $R_1 = 1\Omega$, $R_2 = 10\Omega$, $C_1 = 1mF$, $C_2 = 1\mu F$. Determine the amplitude and the phase of the transfer function in the following regimes

- $\omega \ll \omega_1$
- $\omega_1 \ll \omega \ll \omega_2$
- $\omega_2 \ll \omega$

$$\text{Let } G(s = j\omega) = \frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1} \frac{j \frac{\omega}{\omega_1}}{(1 + j \frac{\omega}{\omega_1})(1 + j \frac{\omega}{\omega_2})}$$

Find:

$$|G(s = j\omega)| \quad \angle G(s = j\omega)$$

- $\omega \ll \omega_1$:

$$\begin{aligned} G(s = j\omega) &= -\frac{R_2}{R_1} \frac{j \frac{\omega}{\omega_1}}{(1 + j0)(1 + j0)} \\ &= -\frac{R_2}{R_1} \left[\frac{j \frac{\omega}{\omega_1}}{1} \right] \\ &= \frac{R_2}{R_1} e^{-j\pi} \left[\frac{\omega}{\omega_1} e^{j\frac{\pi}{2}} \right] \end{aligned}$$

$$= \frac{R_2}{R_1} \frac{\omega}{\omega_1} e^{-\frac{\pi}{2}j}$$

$$|G(s = j\omega)| = \frac{R_2}{R_1} \frac{\omega}{\omega_1} (\approx 0) \quad \angle G(s = j\omega) = -\pi/2$$

- $\omega_1 \ll \omega \ll \omega_2$:

$$\begin{aligned} G(s = j\omega) &= -\frac{R_2}{R_1} \frac{j \frac{\omega}{\omega_1}}{\left(j \frac{\omega}{\omega_1}\right)(1 + j0)} \\ &= -\frac{R_2}{R_1} \left[\frac{j \frac{\omega}{\omega_1}}{j \frac{\omega}{\omega_1} (1)} \right] = -\frac{R_2}{R_1} \\ &= \frac{R_2}{R_1} e^{-\pi j} \end{aligned}$$

$$|G(s = j\omega)| = \frac{R_2}{R_1}$$

$$\angle G(s = j\omega) = -\pi$$

- $\omega_2 \ll \omega$:

$$\begin{aligned} G(s = j\omega) &= -\frac{R_2}{R_1} \frac{j \frac{\omega}{\omega_1}}{\left(j \frac{\omega}{\omega_1}\right)\left(j \frac{\omega}{\omega_2}\right)} \\ &= -\frac{R_2}{R_1} \left[\frac{1}{\left(j \frac{\omega}{\omega_2}\right)} \right] = \frac{R_2}{R_1} \frac{j}{\left(\frac{\omega}{\omega_2}\right)} \\ &= \frac{R_2}{R_1} \left(\frac{\omega}{\omega_2}\right) e^{-\frac{3\pi}{2}j} \end{aligned}$$

$$|G(s = j\omega)| = \frac{R_2}{R_1} \left(\frac{\omega}{\omega_2}\right) (\approx 0)$$

$$\angle G(s = j\omega) = -3\pi/2$$

Question 2

$$R_1 = 1\Omega \quad R_2 = 10\Omega$$

$$C_1 = 1mF \quad C_2 = 1\mu F$$

$$\omega_1 = \frac{1}{R_1 C_1} = 10^3$$

$$\omega_2 = \frac{1}{R_2 C_2} = 10^5$$



$$G(s = j\omega) = \frac{-R_2}{R_1} \frac{j \frac{\omega}{\omega_1}}{(1 + j \frac{\omega}{\omega_1})(1 + j \frac{\omega}{\omega_2})}$$

$$G(s = j\omega) = -10 \frac{j \frac{\omega}{10^3}}{(1 + j \frac{\omega}{10^3})(1 + j \frac{\omega}{10^5})}$$

• $\omega \ll 10^3$

$$|G(s = j\omega)| = \frac{R_2}{R_1} \frac{\omega}{\omega_1} = \frac{1}{10^2} \omega$$

$$20 \lg |G(s = j\omega)| = -40 + 20 \lg \omega$$

$$\angle G(s = j\omega) = -\pi/2$$

• $10^3 \ll \omega \ll 10^5$

$$|G(s = j\omega)| = \frac{R_2}{R_1}$$

$$20 \lg |G(s = j\omega)| = 20 \lg \frac{R_2}{R_1} = 20 \lg \frac{10}{1} = 20$$




$$\angle G(s = j\omega) = -\pi$$

• $10^5 \ll \omega$

$$|G(s = j\omega)| = \frac{R_2}{R_1 \left(\frac{\omega}{\omega_2}\right)} = \frac{10^6}{\omega}$$

$$20 \lg |G(s = j\omega)| = 120 - 20 \lg \omega$$

$$\angle G(s = j\omega) = -3\pi/2$$

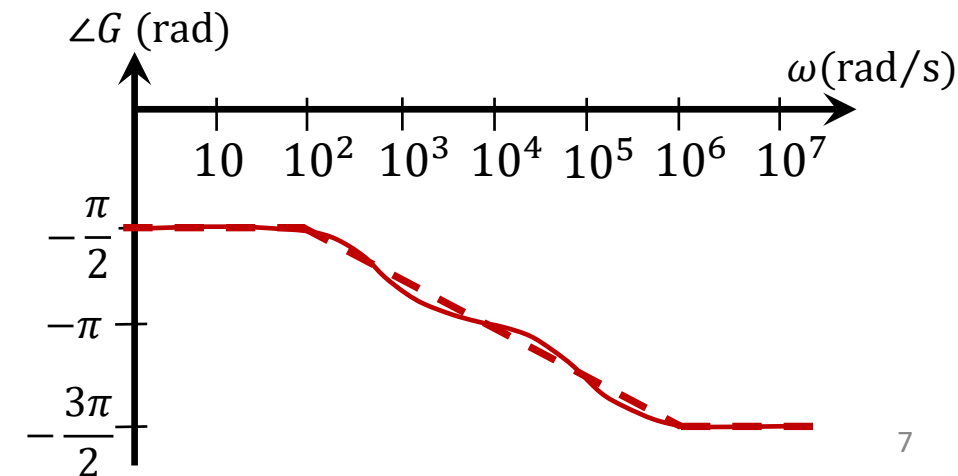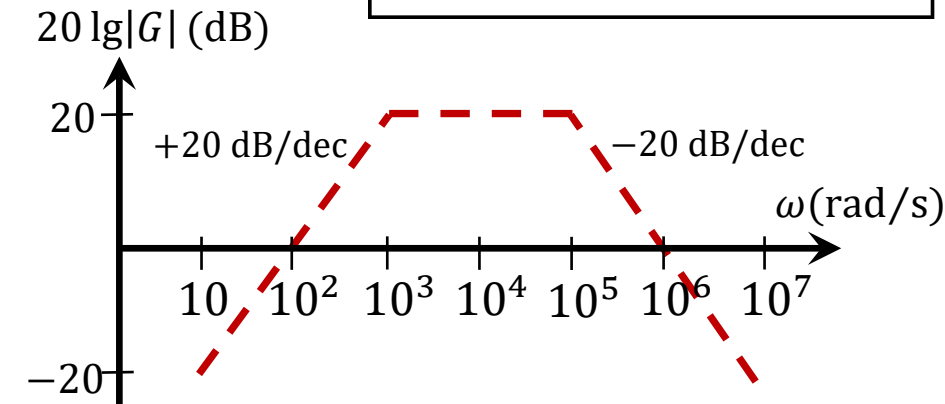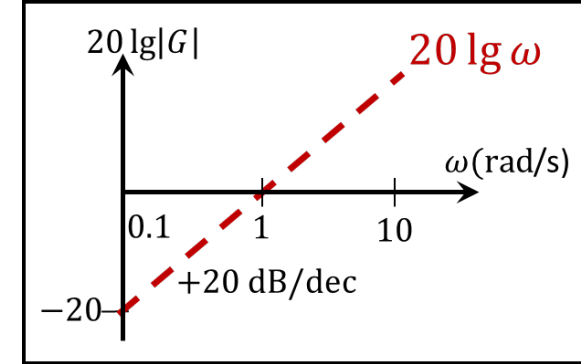

Question 2 EXTRA

Drawing straight lines bode plots

$$G(s = j\omega) = -10 \frac{j \frac{\omega}{10^3}}{\left(1 + j \frac{\omega}{10^3}\right) \left(1 + j \frac{\omega}{10^5}\right)}$$

$$G(s) = -10 \frac{\frac{s}{10^3}}{\left(1 + \frac{s}{10^3}\right) \left(1 + \frac{s}{10^5}\right)}$$




$$G(s) = -10 \frac{\frac{s}{10^3}}{\left(\frac{s + 10^3}{10^3}\right) \left(\frac{s + 10^5}{10^5}\right)}$$



$$G(s) = -\frac{1}{10^2} (s) \left(\frac{10^3}{s + 10^3} \right) \left(\frac{10^5}{s + 10^5} \right)$$

Corner frequencies

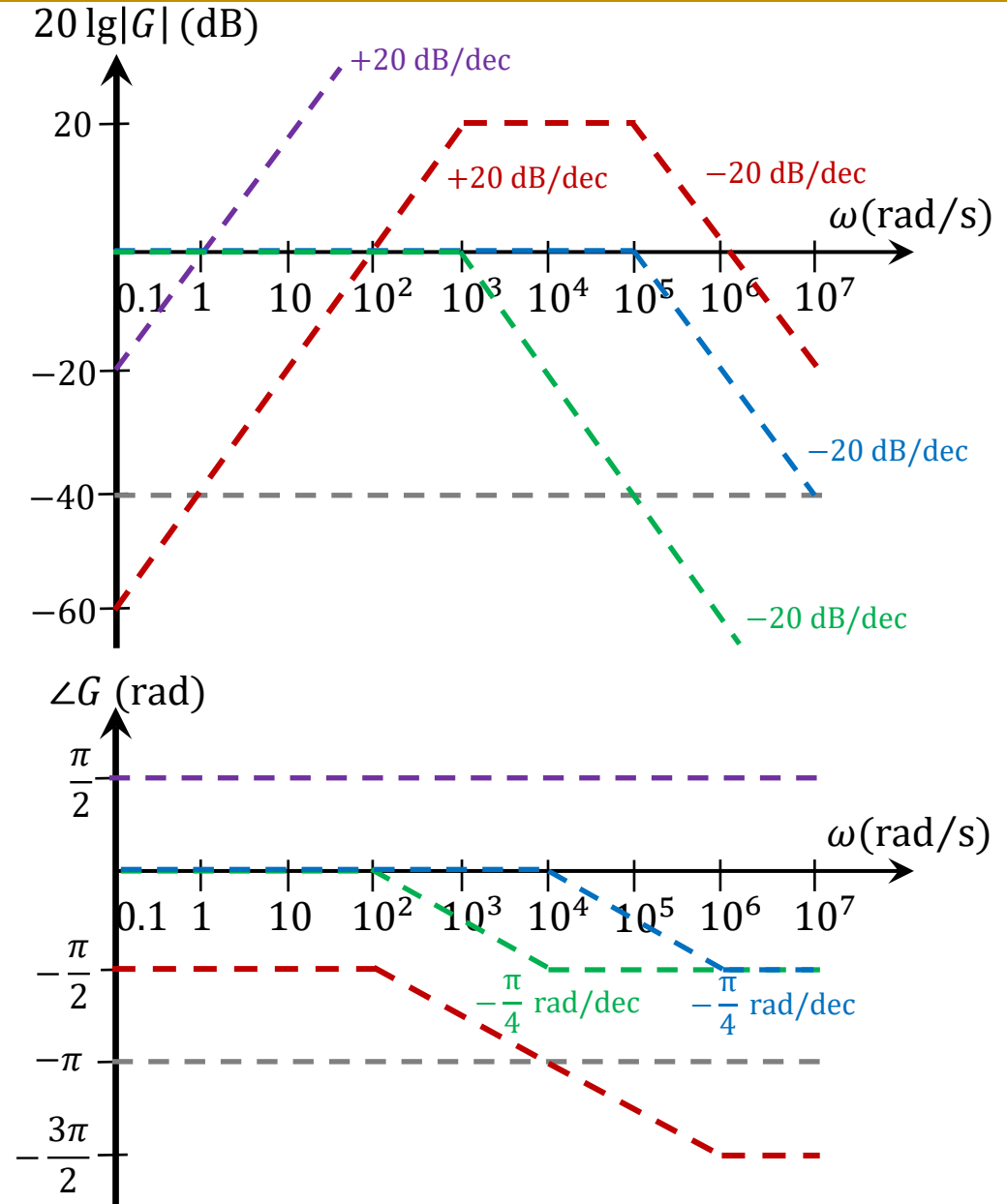

Question 2

3. Determine (approximately) the responses $V_{out}(t)$ of the circuit to the following inputs

- $V_{in}(t) = 5 \sin(10^4 t)$
- $V_{in}(t) = 2 \cos(10t)$
- $V_{in}(t) = 5 \sin(10^4 t) + 2 \cos(10t) - 3 \cos(10^7 t)$

Note:

$$r(t) = r_0 \sin(\omega t) \quad \frac{C}{R} = G(s)$$

$$c(t) = r_0 |G(s = j\omega)| \sin(\omega t + \angle G(s = j\omega))$$

(steady state)

- $V_{in}(t) = 5 \sin(10^4 t)$

$$\omega = 10^4 \Rightarrow \omega_1 \ll \omega \ll \omega_2$$

(within passband)

$$\omega_1 = 10^3 \text{ \& } \omega_2 = 10^5$$

$$\Rightarrow V_{out} = V_{in_0} |G(s = j\omega)| \sin(\omega t + \angle G(s = j\omega))$$

$$= 5(10) \sin(10^4 t + (-\pi))$$

$$= 50 \sin(10^4 t - \pi)$$

$$|G(s = j\omega)| = \frac{R_2}{R_1} = 10$$

$$\angle G(s = j\omega) = -\pi$$

can also be derived graphically
using bode plot (if given)

$$\text{At } \omega = 10^4, 20 \lg |G| = 20$$

$$\lg |G| = 1$$

$$\Rightarrow |G(s = 10^4 j)| = 10$$

$$\angle G(s = j\omega) = -\pi$$

- $V_{in}(t) = 2 \cos(10t)$


$$\omega = 10 \Rightarrow \omega \ll \omega_1$$

$$\Rightarrow V_{out} = V_{in_0} |G(s = j\omega)| \cos(\omega t + \angle G(s = j\omega))$$

$$= 0.2 \cos(10t - \pi/2) \text{ (attenuated)}$$

$$|G(s = j\omega)| = \frac{R_2}{R_1} \frac{\omega}{\omega_1} = 0.1$$

$$\angle G(s = j\omega) = -\pi/2$$

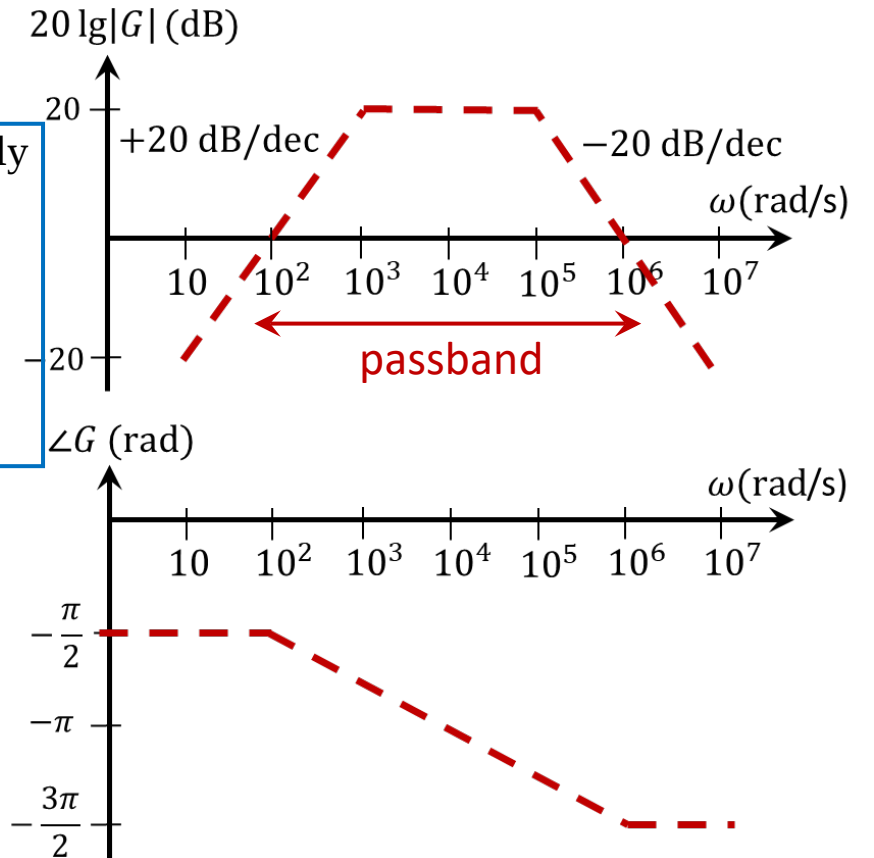

Question 2

3. Determine (approximately) the responses $V_{out}(t)$ of the circuit to the following inputs

- $V_{in}(t) = 5 \sin(10^4 t)$
- $V_{in}(t) = 2 \cos(10t)$
- $V_{in}(t) = 5 \sin(10^4 t) + 2 \cos(10t) - 3 \cos(10^7 t)$

- $V_{in}(t) = 5 \sin(10^4 t) + 2 \cos(10t) - 3 \cos(10^7 t)$

Only the signal at $\omega = 10^4$ will pass (the first term)

$$|G(s = j\omega)| = \frac{R_2}{R_1} = 10 \quad \angle G(s = j\omega) = -\pi$$

$$\begin{aligned} \Rightarrow V_{out} &= V_{in_0} |G(s = j\omega)| \sin(\omega t + \angle G(s = j\omega)) \\ &= 50 \sin(10^4 t - \pi) \end{aligned}$$

Note:

$$\begin{aligned} r(t) &= r_0 \sin(\omega t) & \frac{C}{R} &= G(s) \\ c(t) &= r_0 |G(s = j\omega)| \sin(\omega t + \angle G(s = j\omega)) & & \\ & \text{(steady state)} & & \end{aligned}$$

